

**BRAC University**  
 Department of Electrical & Electronic Engineering  
 Assignment 1a, Summer 2025  
 EEE/ECE203: Electrical Circuits II

**Total Marks: 100**

---

**Q1. [20 marks]**

Obtain the rms values of the waveforms shown in the Fig. 1a and 1b.

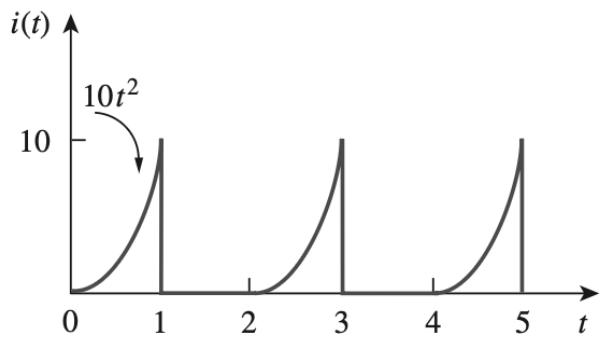


Figure 1a

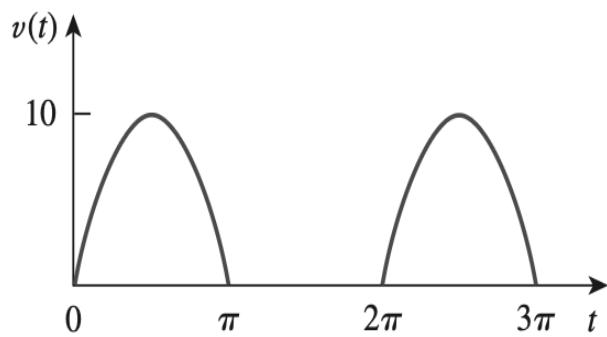


Figure 1b

**Q2. [20 marks]**

For the network in Fig. 2:

- Find the total impedance  $Z_T$ .
- Find the source current  $\mathbf{I}_s$  in phasor form.
- Find the currents  $\mathbf{I}_1$  and  $\mathbf{I}_2$  in phasor form.
- Find the voltages  $\mathbf{V}_1$  and  $\mathbf{V}_{ab}$  in phasor form.
- Find the average power delivered to the network.
- Draw the phasor diagram.

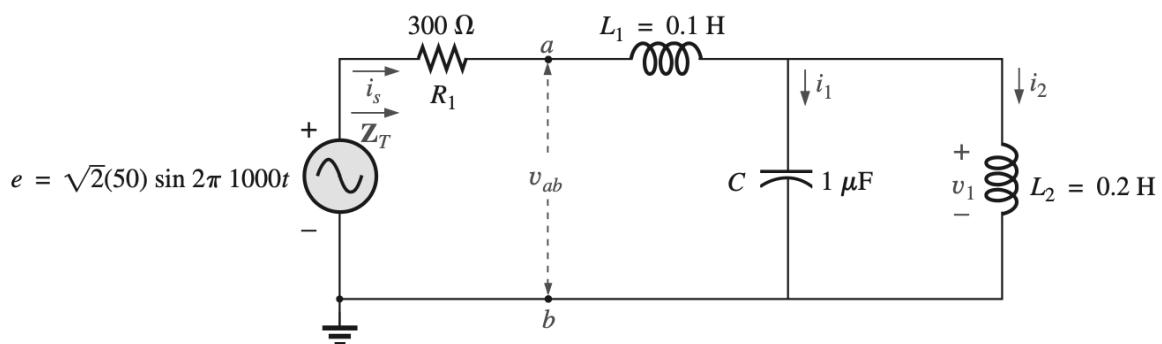


Figure 2

**Q3. [20 marks]**

For the network of Fig. 3:

- Find the total impedance  $Z_T$ .
- Find the voltage  $V_1$ ,  $V_2$ , and  $V_3$  in phasor form.
- Find the current  $I_1$  in phasor form.
- Find the source voltage  $V_s$  in phasor form.
- Find the average power delivered to the network.
- Draw the phasor diagram.

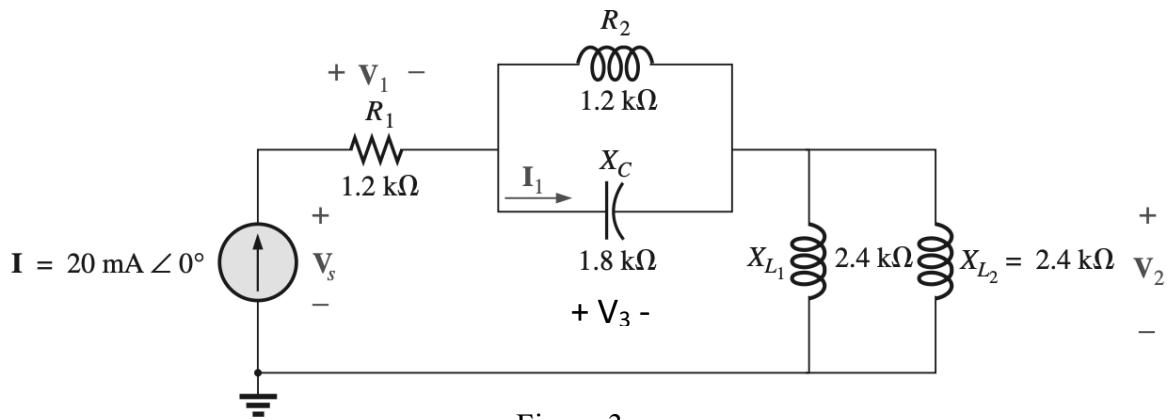


Figure 3

**Q4. [10 marks]**

Find the instantaneous power supplied by the source in the network in Fig. 4.

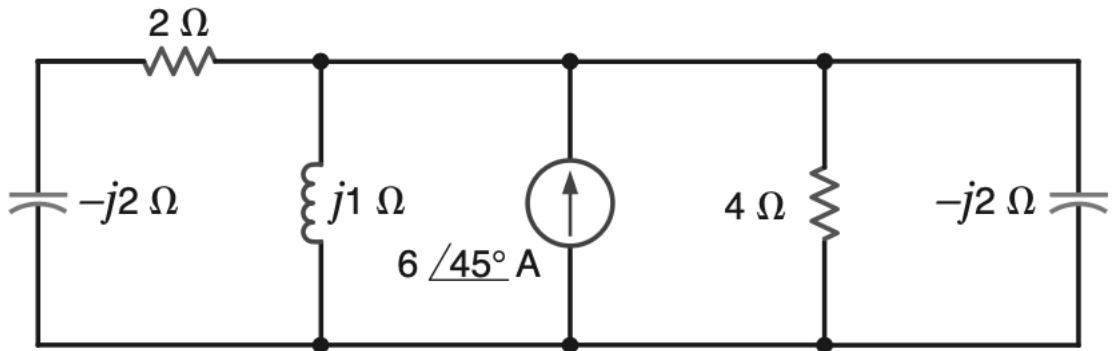


Figure 4

**Q5. [10 marks]**

Find the impedance,  $Z$ , for the network in Fig. 5.

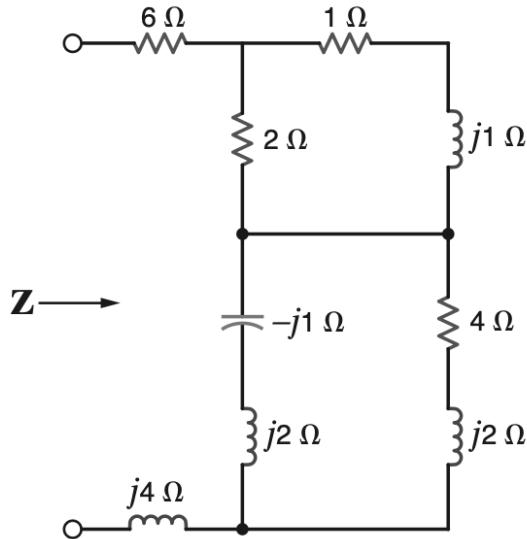


Figure 5

**Q6. [10 Marks]**

Find  $v_x(t)$  for the circuit shown in Fig. 6.

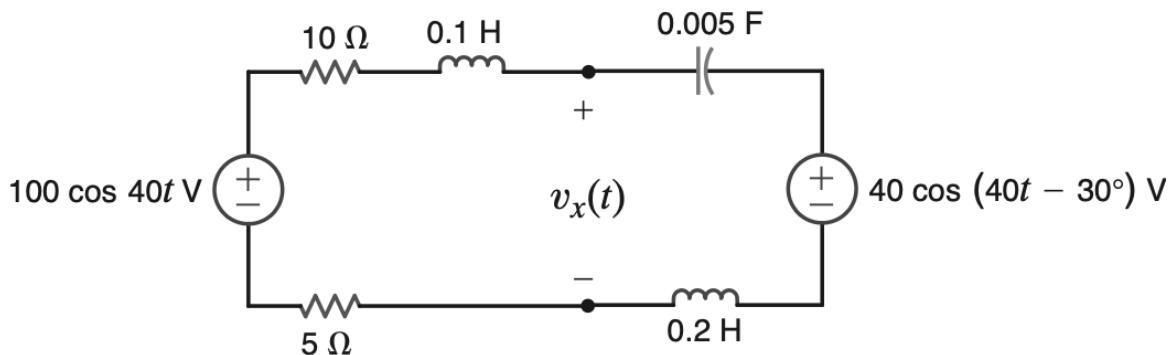


Figure 6

**Q7. [10 Marks]**

Find the phase relationship between the following waveforms:

- (a)  $v(t) = 2 \cos(\omega t - 30^\circ)$ ,  $i(t) = 5 \sin(\omega t + 60^\circ)$
- (b)  $v(t) = -4 \cos(\omega t + 90^\circ)$ ,  $i(t) = -2 \sin(\omega t + 10^\circ)$

EEE 203

Assignment 1 a.

Name: Souvik Barman Ratum

ID : 24121205

Section: 06

Ans to the Q. No - 1figure 1a  $\Rightarrow$ 

$$i_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$\Rightarrow i_{rms} = \sqrt{\frac{1}{5} \left[ \int_0^1 (20t^2)^2 dt + \int_1^2 (20t^2)^2 dt + \int_2^3 (20t^2)^2 dt \right]}$$

$$= \sqrt{\frac{1}{5} \left[ \frac{100}{5} [t^5]_0^1 + \frac{100}{5} [t^5]_1^2 + \frac{100}{5} [t^5]_2^3 \right]}$$

$$= \sqrt{\frac{1}{5} \left[ 20 \times (1^5 - 0) + 20 \times (3^5 - 2^5) + 20 \times (5^5 - 4^5) \right]}$$

$$= \sqrt{\frac{1}{5} \left[ 20 + (20 \times 211) + (20 \times 2101) \right]}$$

$$= 96.187 A \quad \underline{\text{Ans}}$$

figure 1b,

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$\Rightarrow \sqrt{\frac{1}{3\pi} \left[ \int_0^{\pi} (10\sin t)^2 dt + \int_{\pi}^{3\pi} (10\sin t)^2 dt \right]}$$

$$\Rightarrow \sqrt{\frac{1}{3\pi} \left[ \int_0^{\pi} 100\sin^2 t dt + \int_{\pi}^{3\pi} 100\sin^2 t dt \right]}.$$

now,

$$\begin{aligned}
 \int 100 \sin^2 t dt &= 100 \int \frac{1}{2} (1 - \cos 2t) dt \\
 &= 100 \times \frac{1}{2} \times \left[ \int dt - \int \cos 2t dt \right] \\
 &= 50 \cdot t - 50 \cdot \frac{\sin 2t}{2} \\
 &= 50t - 25 \sin 2t
 \end{aligned}$$

$$\therefore \int_0^\pi 100 \sin^2 t dt = 50 [t]_0^\pi - 25 [\sin 2t]_0^\pi = 50\pi$$

$$\int_{2\pi}^{3\pi} 100 \sin^2 t dt = 50 [t]_{2\pi}^{3\pi} - 25 [\sin 2t]_{2\pi}^{3\pi} = 50\pi$$

now,


$$V_{rms} = \sqrt{\frac{1}{3\pi} \left[ \int_0^\pi 100 \sin^2 t dt + \int_{2\pi}^{3\pi} 100 \sin^2 t dt \right]}$$

$$= \sqrt{\frac{1}{3\pi} [50\pi + 50\pi]}$$

$$= \sqrt{\frac{1}{3\pi} (100\pi)}$$

$$= 5.77 \cdot V$$

Ans

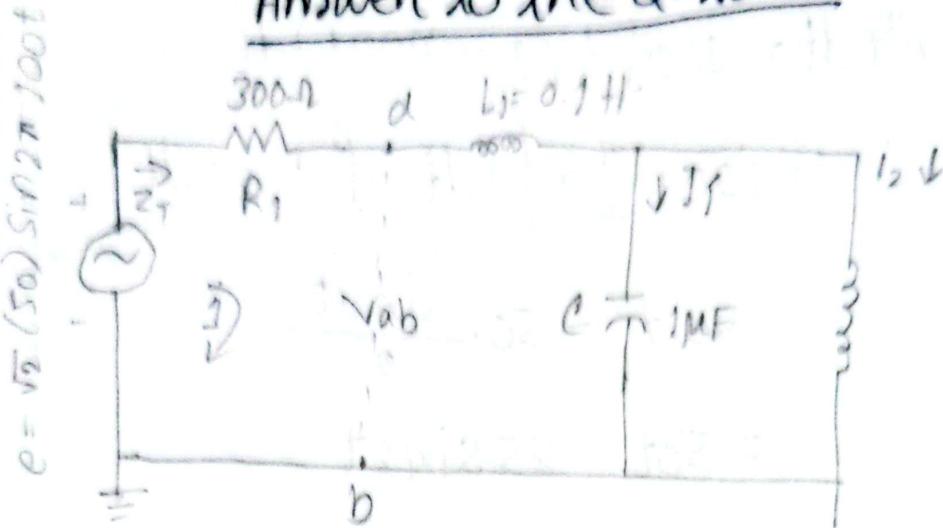Answer to the Q. No-2

$$Z_{R_1} = 300 \angle 0^\circ, E = 50\sqrt{2} \angle 0^\circ$$

$$Z_C = \frac{1}{2\pi \cdot 1000 \cdot 1 \times 10^{-6}} \angle -90^\circ = 159,155 \angle -90^\circ$$

$$Z_{L_1} = \frac{2\pi \cdot 1000 \times 0.1}{1} \angle 90^\circ = 628,319 \angle 90^\circ$$

$$Z_{L_2} = \frac{2\pi \times 1000 \times 0.2}{1} \angle 90^\circ = 1256.637 \angle 90^\circ$$

$$Z_t = \frac{Z_C \cdot Z_{L_2}}{Z_C + Z_{L_2}} = 182.23 \angle -90^\circ$$

$$Z_t = Z_1 + Z_{R_1} + Z_{L_1} = 537.58 \angle 56.07^\circ$$

$$i_S = \frac{E}{Z_t}$$

$$= \frac{50\sqrt{2} \angle 0^\circ}{537.58 \angle 56.07^\circ} = 0.131 \angle -56.07^\circ$$

Applying KVL at loop P 1  $\Rightarrow$

$$-e + V_{R_1} + V_{ab} = 0$$

$$\Rightarrow V_{ab} = e - V_{R_1}$$

$$\Rightarrow V_{ab} = 50\sqrt{2} \angle 0^\circ - \{(0.131 \angle -56.07) \times (300 \angle 0^\circ)\}$$

$$\Rightarrow V_{ab} = V_a = 58.67 \angle 33.76^\circ$$

now,

$$V_a - V_c = i_S Z_L$$

$$\Rightarrow V_c = V_a - i_S Z_L$$

$$\Rightarrow V_{ac} = V_c \angle 23^\circ$$

$$\Rightarrow V_c = 58.67 \angle 33.76^\circ - \{(0.131 \angle -56.07) \times (628.39 \angle 90^\circ)\}$$

$$V_c = 23.64 \angle -145.65^\circ$$

$$V_c = V_s = 23.64 \angle -145.65^\circ$$

now,

a] Total impedance  $Z_T = 537.58 \angle 56.07^\circ$

b]  $I_g = 0.131 \angle -56.07^\circ$

c)  $I_s = \frac{V_c}{Z_L} = \frac{23.64 \angle -145.65^\circ}{159.154 \angle -90^\circ}$

$$= 0.1485 \angle -55.65^\circ$$

$$J_1 = \frac{V_c}{Z_L} = \frac{23.64 \angle -145.65^\circ}{1256.637 \angle 90^\circ} = 0.0188 \angle 124.35^\circ$$

d)  $V_1 = 23.64 \angle -145.65^\circ$


$$V_{ab} = 58.67 \angle 33.76^\circ$$

e)  $P_{av} = \frac{V_m \cdot I_m}{2} \cos(\theta_V - \theta_i)$


$$= \frac{50\sqrt{2} \times 0.131}{2} \cos(0 + 56.07^\circ)$$

$$= 2.585 \text{ watt}$$

f)

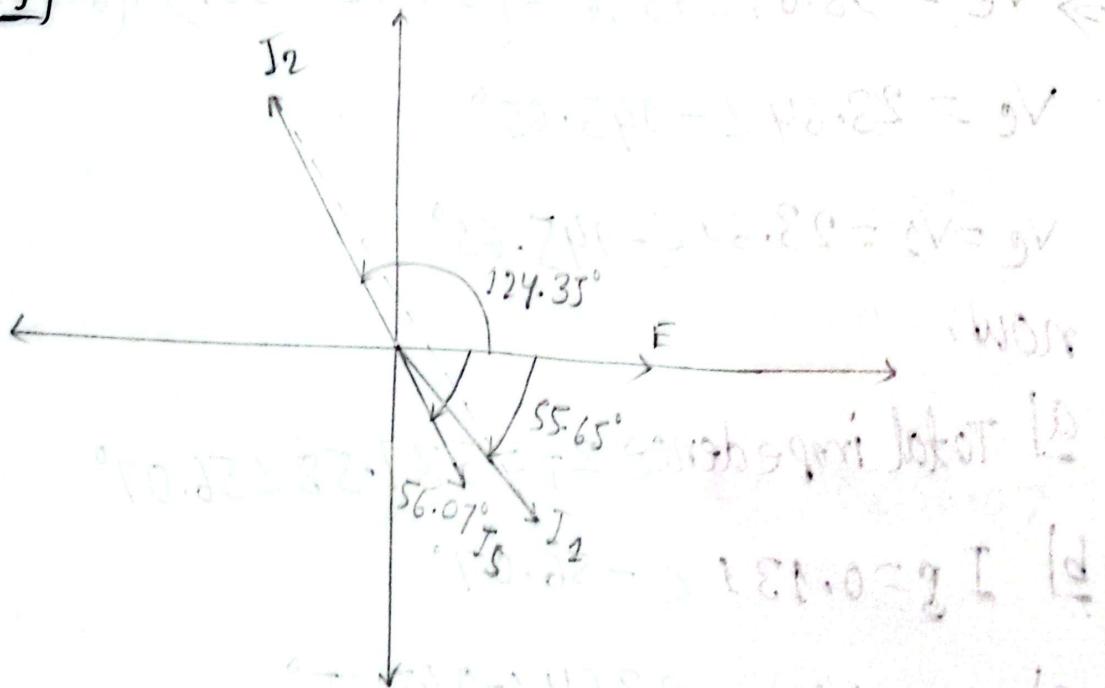

Ans to the Q. NO - 3

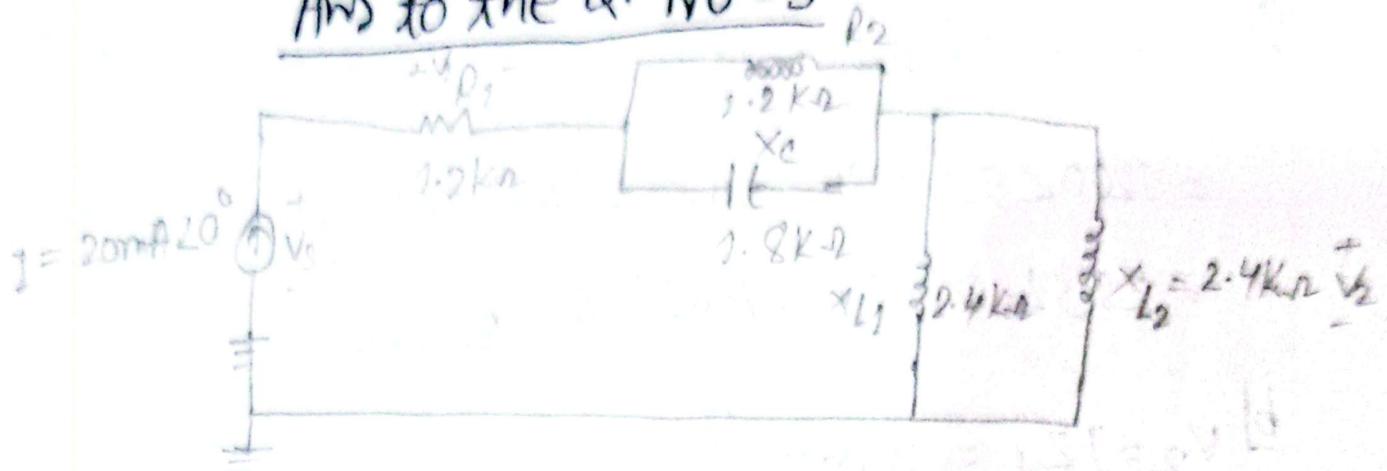

$$Z_{R1} = 1200 \angle 0^\circ \Omega, \quad Z_{R2} = 1200 \angle 0^\circ \Omega$$

$$Z_C = 1800 \angle -90^\circ \Omega, \quad Z_{L1} = 2400 \angle 90^\circ \Omega$$

$$Z_{L2} = 2400 \angle 90^\circ \Omega$$

$Z_{L1}$  and  $Z_2$  are in parallel.

$$Z_{P1} = \frac{Z_{L1} \cdot Z_{L2}}{Z_{L1} + Z_{L2}} = \frac{2400 \angle 90^\circ \times 2400 \angle 90^\circ}{2400 \angle 90^\circ + 2400 \angle 90^\circ}$$

$$= 1200 \angle 90^\circ \Omega$$

$Z_{R2}, Z_C$  are in parallel,

$$Z_{P2} = \frac{Z_{R2} \cdot Z_C}{Z_{R2} + Z_C} = \frac{1200 \angle 0^\circ \times 1800 \angle -90^\circ}{1200 \angle 0^\circ + 1800 \angle -90^\circ}$$

$$= 998.46 \angle -33.0^\circ \Omega$$

$Z_{P1}, Z_{P2}$  and  $Z_{R1}$  are in series.

a]  $Z_T = Z_{P1} + Z_{P2} + Z_{R1}$

$$= 1200 \angle 90^\circ + 998.46 \angle -33.69^\circ + 1200 \angle 0^\circ$$

$$= 2131.089 \angle 17.65^\circ \text{ Ans}$$

b]

$$V_2 = IZ_1 = 20 \times 10^{-3} \angle 0^\circ \times 1200 \angle 90^\circ$$

$$= 24 \angle 90^\circ \text{ V. Ans}$$

$$V_3 = IZ_2 = 20 \times 10^{-3} \angle 0^\circ \times 998.46 \angle -33.69^\circ$$

$$= 19.96 \angle -33.69^\circ \text{ Ans}$$


$$V_1 = IZ_{R1} = 20 \times 10^{-3} \angle 0^\circ \times 1200 \angle 0^\circ$$

$$= 24 \angle 0^\circ \text{ V Ans}$$

c]  $I_1 = \frac{V_3}{Z_C} = \frac{19.96 \angle -33.69^\circ}{j800 \angle -90^\circ}$

$$= 0.011 \angle 56.31^\circ \text{ Ans}$$

d)

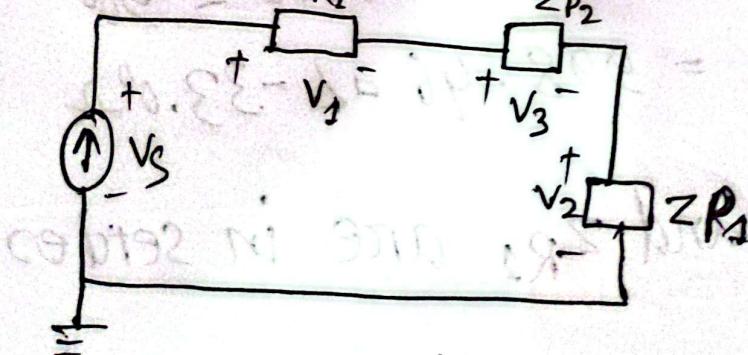

Applying KVL,

$$-V_s + V_1 + V_3 + V_2 = 0$$

$$\Rightarrow V_s = V_1 + V_2 + V_3 = 0$$

$$= 24 \angle 0^\circ + 24 \angle 90^\circ + 19.96 \angle -33.66^\circ$$


$$= 42.616 \angle 17.66^\circ \text{ Ans}$$

$\therefore P_{av} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$


$$= \frac{42.616 \times 0.02}{2} \cos(17.66^\circ - 0^\circ)$$

$$\approx 0.41 \text{ watt}$$

f)

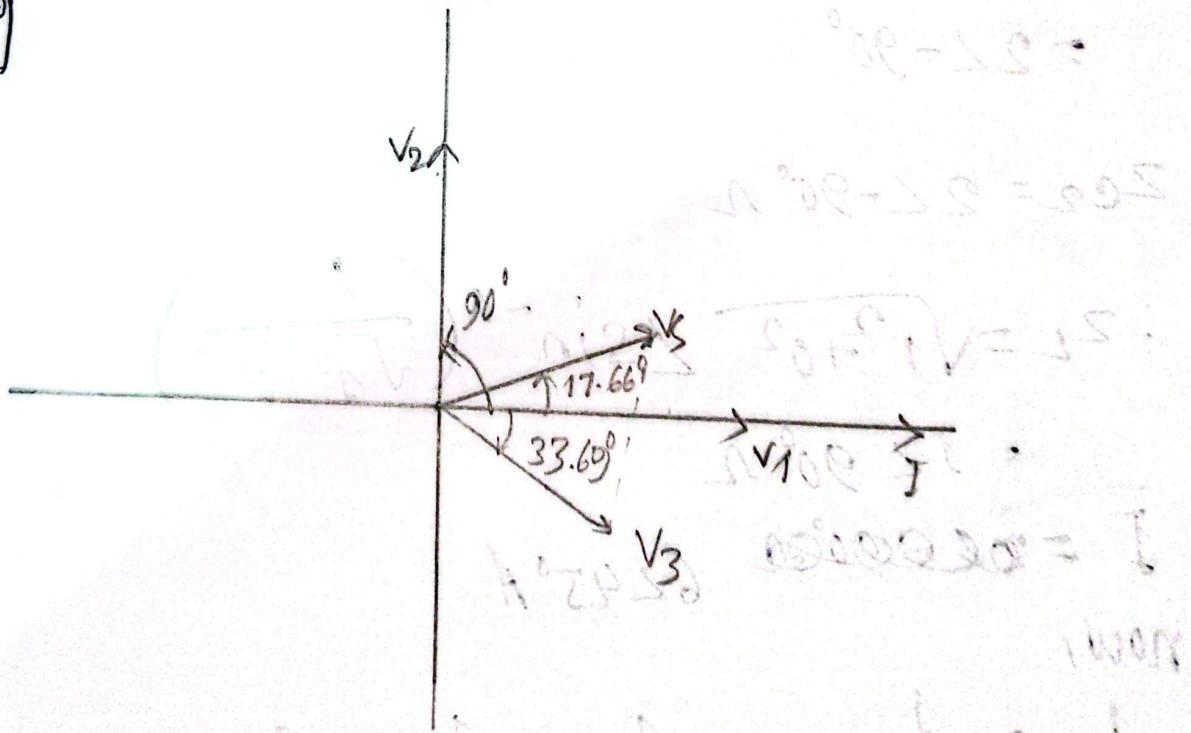

Ans to the Q. No-4

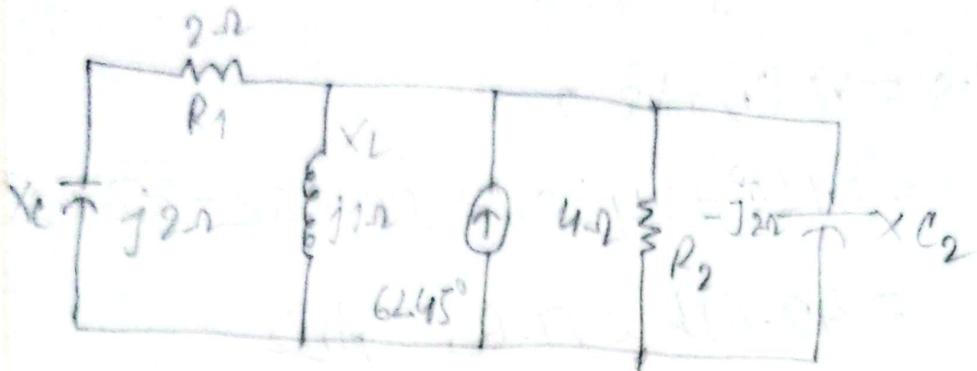

$$Z_{R_2} = 4 \angle 0^\circ, Z_R = 2 \angle 0^\circ \Omega$$

$$X_{C_1} = -j2\Omega, X_L = j1\Omega$$

$$\begin{aligned} Z_{C_1} &= \sqrt{0^2 + (-2)^2} \angle \sin^{-1}\left(\frac{-2}{\sqrt{0^2 + (-2)^2}}\right) \\ &= 2 \angle -90^\circ \Omega \end{aligned}$$

$$Z_{C_2} = 2 \angle -90^\circ \Omega$$

$$\begin{aligned} \therefore Z_L &= \sqrt{1^2 + 0^2} \angle \sin^{-1}\left(\frac{1}{\sqrt{1^2 + 0^2}}\right) \\ &= 1 \angle 90^\circ \Omega \end{aligned}$$

$$I = 2 \angle 0^\circ \text{ A} \quad 6 \angle 45^\circ \text{ A}$$

now,

$$\frac{1}{Z_T} = \frac{1}{Z_{R_1} + Z_{C_1}} + \frac{1}{Z_L} + \frac{1}{2R_2} + \frac{1}{2C_2}$$

$$\frac{1}{Z_T} = \frac{1}{2 \angle 0^\circ + 2 \angle -90^\circ} + \frac{1}{1 \angle 90^\circ} + \frac{1}{4 \angle 0^\circ} + \frac{1}{2 \angle -90^\circ}$$

$$Z_T = \frac{1}{0.56 \angle -26.57^\circ} \Omega$$

$$= 1.79 \angle 26.57^\circ \Omega$$

$$V = I Z_T = 6 \angle 45^\circ \times 1.79 \angle 26.57^\circ \Omega$$

$$= 10.74 \angle 71.57^\circ V$$

$$i(t) = 6 \sin(\omega t + 45^\circ)$$

$$v(t) = 10.74 \sin(\omega t + 71.57^\circ)$$

now.


$$P(t) = i(t)v(t) = 6 \sin(\omega t + 45^\circ) \times 10.74 \sin(\omega t + 71.57^\circ)$$

$$\Rightarrow P(t) = 64.44 \times \frac{1}{2} \times [\cos(\omega t + 45^\circ - \omega t - 71.57^\circ) - \cos(\omega t + 45^\circ + \omega t + 71.57^\circ)]$$

$$\Rightarrow P(t) = 32.22 [\cos(-26.57^\circ) - \cos(2\omega t + 116.57^\circ)]$$

$$= 28.82 - \cos(2\omega t + 116.57^\circ)$$

Ans

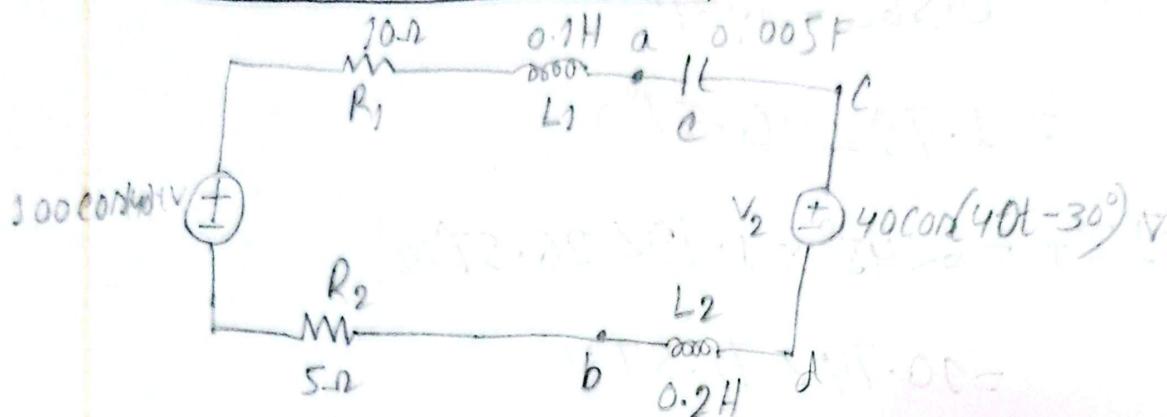Ans to the Q. NO-6

$$Z_{R_1} = 10 \angle 0^\circ, Z_{R_2} = 5 \angle 0^\circ, Z_{L_1} = 40 \times 0.1 \angle 90^\circ$$

$$Z_{L_2} = 40 \times 0.2 \angle 90^\circ = 8 \angle 90^\circ, Z_C = \frac{1}{40 \times 0.005} \angle -90^\circ = 5 \angle -90^\circ$$

$$V_1 = 100 \angle 0^\circ \text{ V}$$

$$V_2 = 40 \angle -30^\circ \text{ V}$$

Applying KVL

$$V_1 + Z_{R_1} I + Z_{L_1} I + Z_C I + V_2 + Z_{L_2} I + Z_{R_2} I = 0$$

$$\Rightarrow I(Z_{R_1} + Z_{L_1} + Z_C + Z_{L_2} + Z_{R_2}) = V_1 - V_2$$

$$\Rightarrow I \times (16.55 \angle 25.02^\circ) = 68.35 \angle 17.07^\circ$$

$$I = 4.13 \angle -8.07^\circ$$

Applying KVL around loop-1,


$$-V_1 + V_{R_1} + V_{L_1} + V_C + V_{R_2} = 0$$

$$\Rightarrow V_x = V_1 - V_{R1} - V_{L1} - V_{R2}$$

$$\Rightarrow V_x = 100 \angle 0^\circ - (10 \angle 0^\circ) \times (4.13 \angle -8.01^\circ) - (4 \angle 90^\circ) (4.13 \angle 8.01^\circ)$$

$$= 37.17 \angle -72^\circ$$

$$v_x(t) = 37.17 \cos(40t - 52^\circ)$$

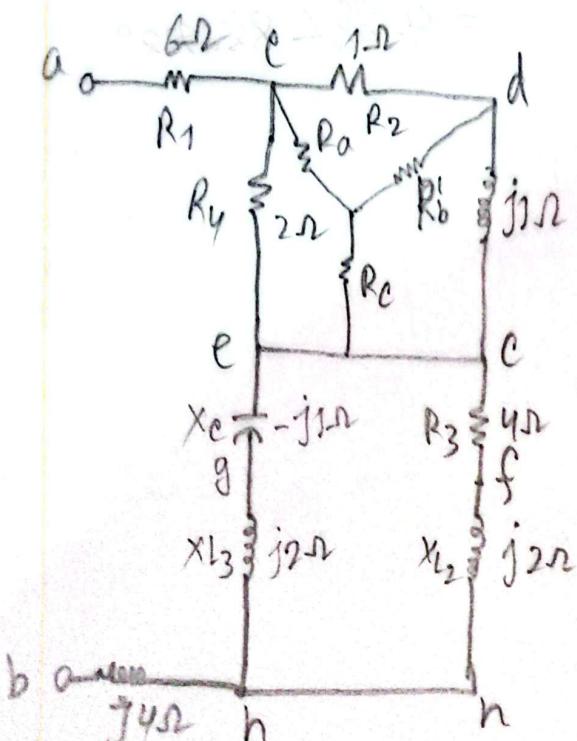AnsAns to the Q. No - 5

$$Z_{R1} = 6 \angle 0^\circ \Omega$$

$$Z_{R2} = 1 \angle 0^\circ \Omega$$

$$Z_{R3} = 4 \angle 0^\circ \Omega$$

$$Z_{R4} = 2 \angle 0^\circ \Omega$$

$$Z_C = \sqrt{0^2 + (-1)^2} \angle \sin^{-1}\left(\frac{-1}{\sqrt{0^2 + (-1)^2}}\right)$$

$$\Rightarrow Z_C = 1 \angle -90^\circ$$

$$Z_{L1} = 1 \angle 90^\circ \Omega$$

$$Z_{L2} = 2 \angle 90^\circ \Omega$$

$$Z_{L3} = 4 \angle 90^\circ \Omega$$

$$Z_{L4} = 4 \angle 90^\circ \Omega$$

$Z_C$  and  $Z_{L3}$  are in series  $Z_{S1} = Z_C + Z_{L3} = 1 \angle 90^\circ \Omega$

$Z_{R3}$  and  $Z_{L2}$  are in parallel  $Z_{S2} = Z_{R3} + Z_{L2}$


$$= 4.47 \angle 26.57^\circ \Omega$$

$Z_{S1}$  and  $Z_{S2}$  are in parallel  $Z_{P1} = \frac{Z_{S1} \times Z_{S2}}{Z_{S1} + Z_{S2}}$

$$= 0.89 \angle 79.69^\circ$$

$Z_P1$  and  $Z_{L4}$  are in series  $Z_{S3} = Z_{P1} + Z_{L4}$

$$= 4.88 \angle 88.122^\circ$$

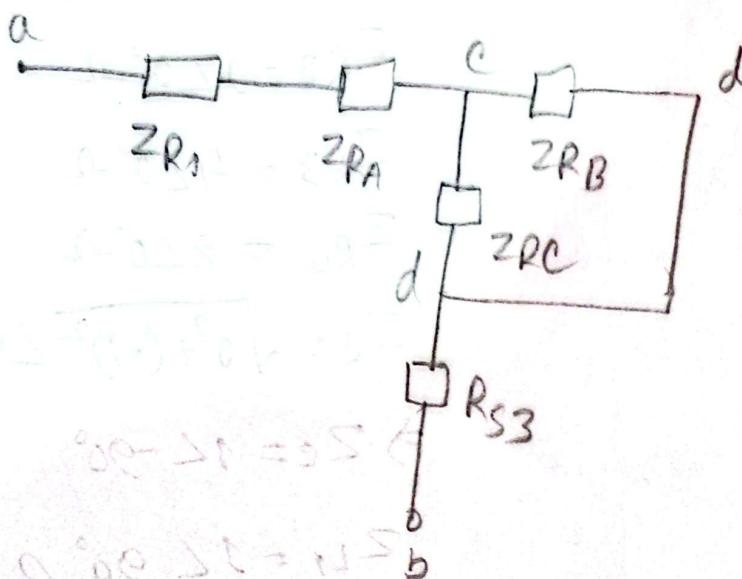

$$Z_{PA} = \frac{Z_{R2} \times Z_{R4}}{Z_{R2} + Z_{R4} + Z_{L1}} = 0.63 \angle -018.435^\circ \Omega$$

$$Z_{RB} = \frac{Z_{R2} \times Z_{R4}}{Z_{R2} + Z_{R4} + Z_{RL1}} = 0.32 \angle 75.57^\circ \Omega$$

$$Z_{RC} = \frac{Z_{R_4} * Z_{RL}}{Z_{R_2} + Z_{R_4} + Z_{R_3}} = 0.63 \angle 71.57^\circ \Omega$$

$Z_{R_1}$  and  $Z_{RA}$  are in series,

$$\begin{aligned} Z_{S4} &= Z_{R_1} + Z_{RA} = 6 \angle 0^\circ + 0.63 \angle -18.435^\circ \\ &= 6.60 \angle -1.73^\circ \Omega \end{aligned}$$

$Z_{RC}$  and  $Z_{RB}$  are in parallel.

$$\begin{aligned} Z_{P3} &= \frac{Z_{RC} \times Z_{RB}}{Z_{RC} + Z_{RB}} = \frac{0.63 \angle 71.57^\circ \times 0.32 \angle 71.57^\circ}{0.63 \angle 671.57^\circ + 0.32 \angle 71.57^\circ} \\ &= 0.21 \angle 71.57^\circ \Omega \end{aligned}$$

Now,


$Z_{P3}$ ,  $Z_{S3}$  and  $Z_{S4}$  are in series,

$$\begin{aligned} Z_T &= Z_{P3} + Z_{S3} + Z_{S4} = 0.22 \angle 71.57^\circ + 4.88 \angle 88.122^\circ \\ &\quad + 6.60 \angle -1.73^\circ \\ &= 8.4 \angle 35.60^\circ \Omega \quad \text{And} \end{aligned}$$

Answer to the Q. No-07...

a)
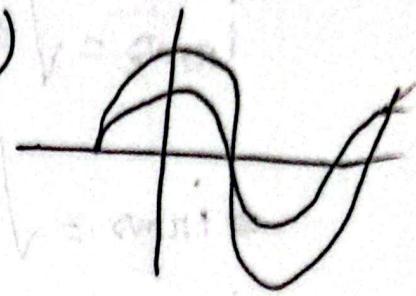
$$\begin{aligned}
 v(t) &= 2 \cos(\omega t - 30^\circ) \\
 &= 2 \sin(\omega t - 30^\circ + 90^\circ) \\
 &= 2 \sin(\omega t + 60^\circ) \\
 i(t) &= 5 \sin(\omega t + 60^\circ)
 \end{aligned}$$



$i(t)$  and  $v(t)$  are in phase.

b)

$$\begin{aligned}
 v(t) &= -4 \cos(\omega t + 90^\circ) \\
 &= -4 \sin(\omega t + 90^\circ - 90^\circ) \\
 &= -4 \sin(\omega t + 0^\circ)
 \end{aligned}$$

$$i(t) = -2 \sin(\omega t + 10^\circ)$$

$v(t)$  lags  $i(t)$  by  $10^\circ$

$i(t)$  leads  $v(t)$  by  $10^\circ$

