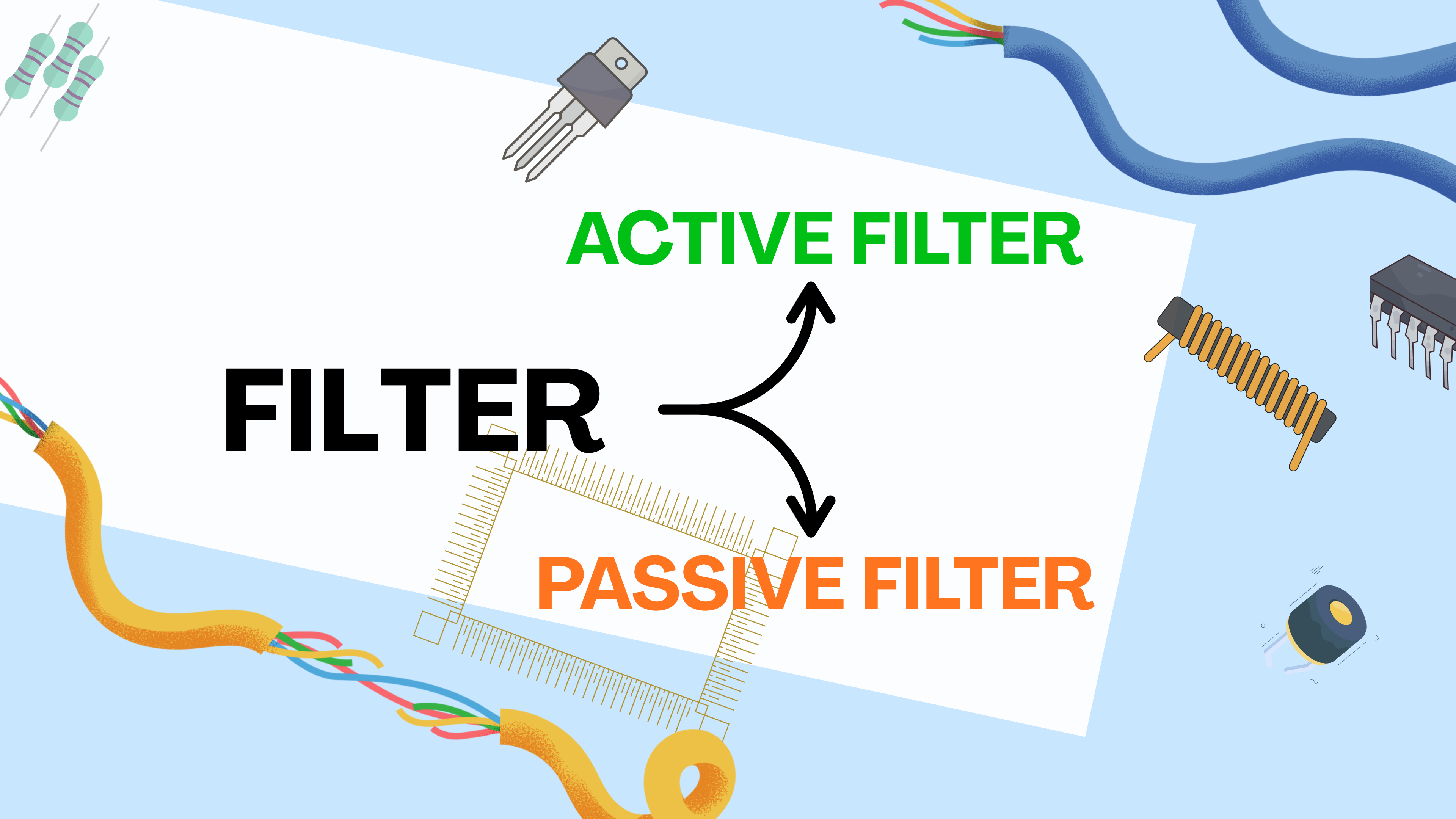




EEE203L

LAB



PROJECT



FILTER

ACTIVE FILTER

PASSIVE FILTER

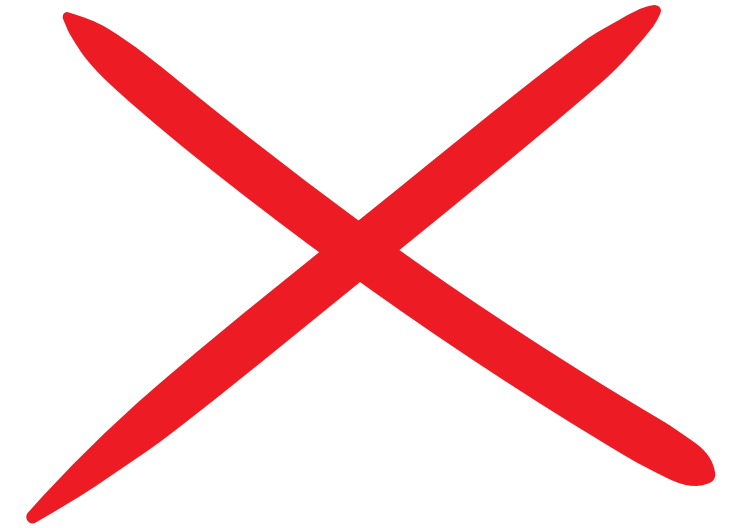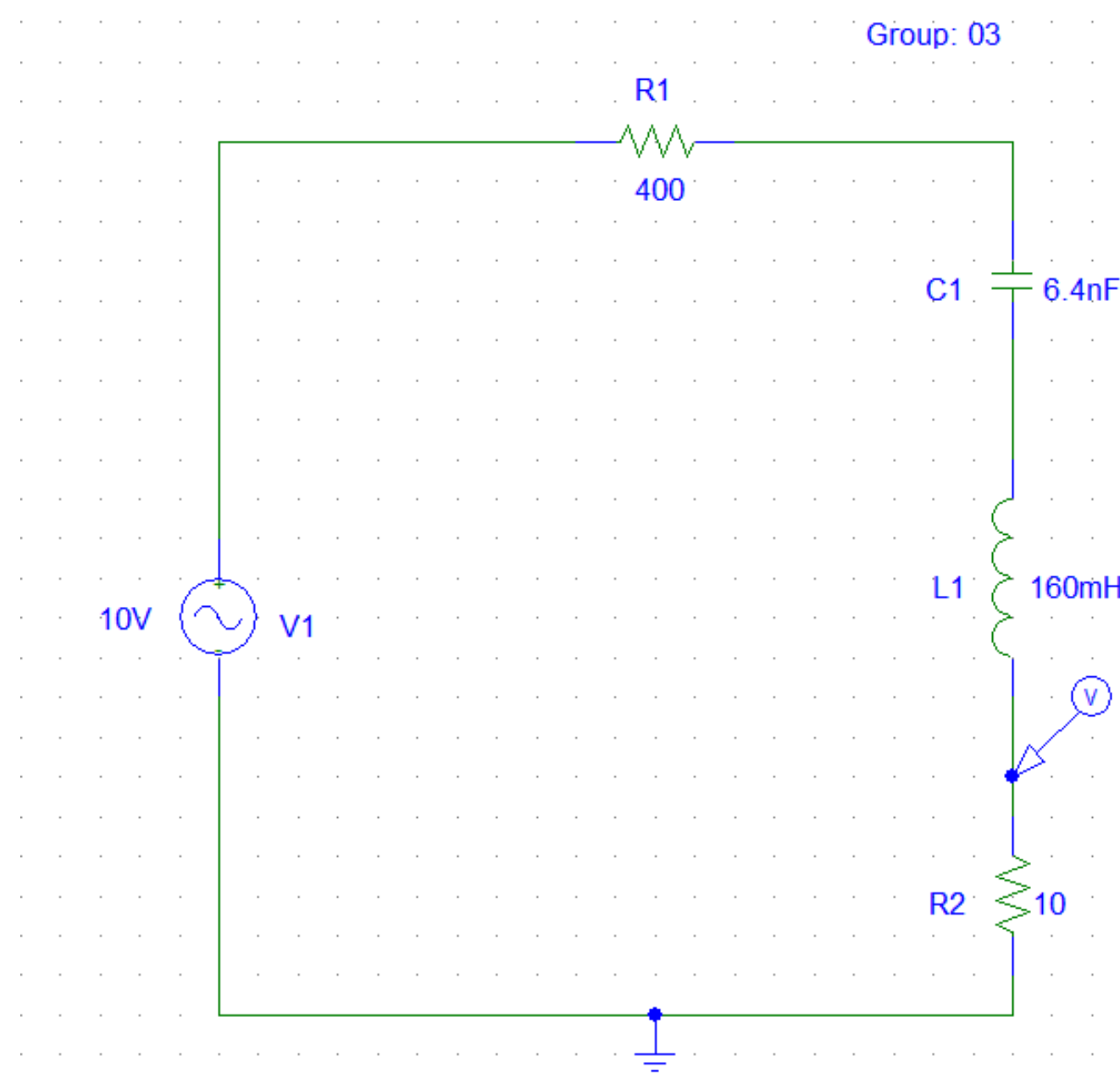

Passive Filter

Resistor (R), Inductor (L), and Capacitor (C).

Do not need an external power supply.

Example: Series RLC circuit .

Active Filter

R, L, C + active components like Operational Amplifiers

Transistors

Need a DC power supply to operate.

Example: Op-Amp based Low-Pass or High-Pass filters.

Building the circuit


Source: 10 Volt AC voltage source.

Resistors: 2 resistors , R1 at 400 ohms and R2 at 10 ohms.

Capacitors: 6.4 nano Farrad capacitor.

Inductor: 160 milli Henry inductor.


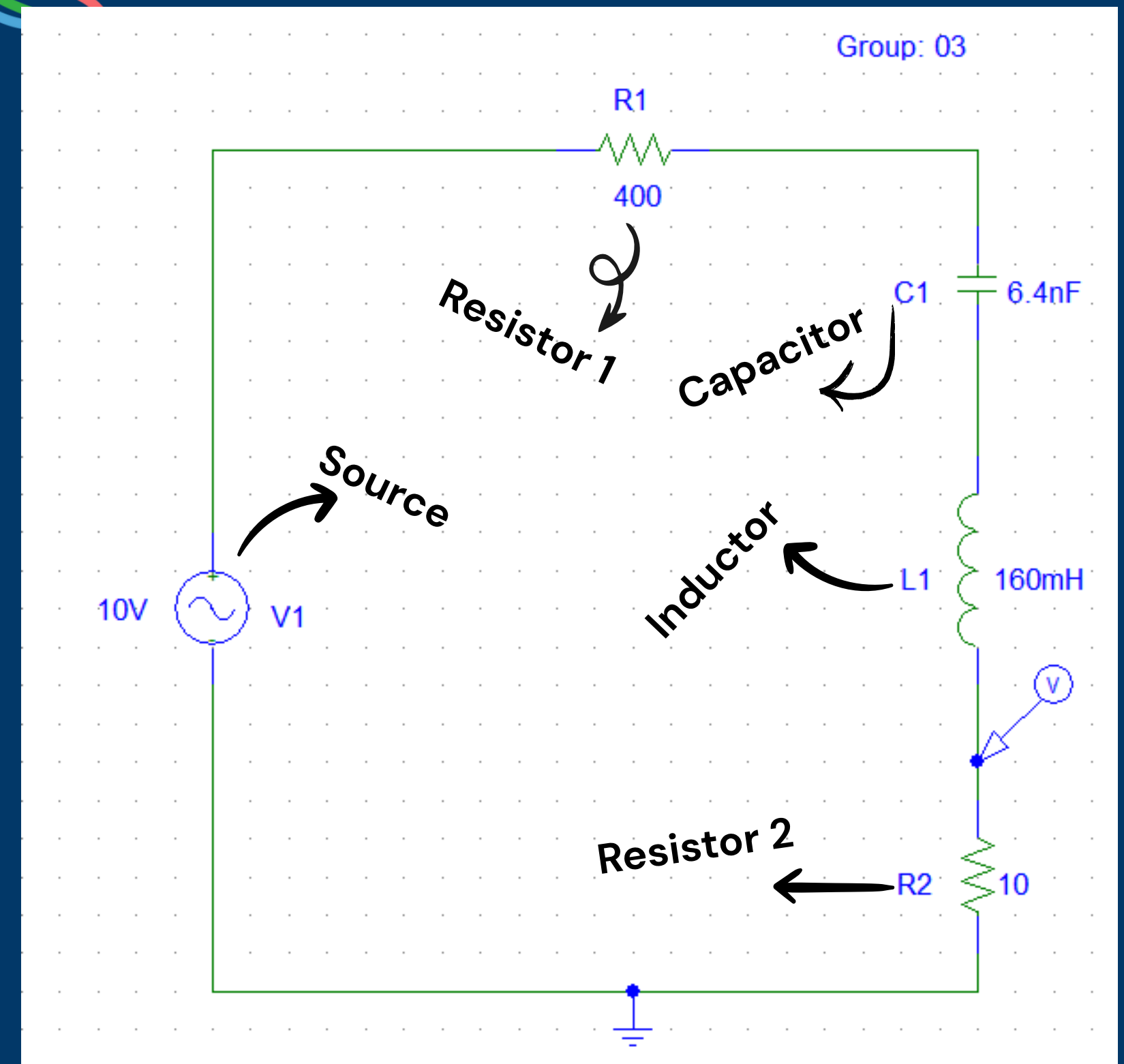
Every element is connected in series, ensuring equal current flow through the circuit.



Rechecking the parameters

1.Ensuring the values of the elements:




2.setting up the simulation:

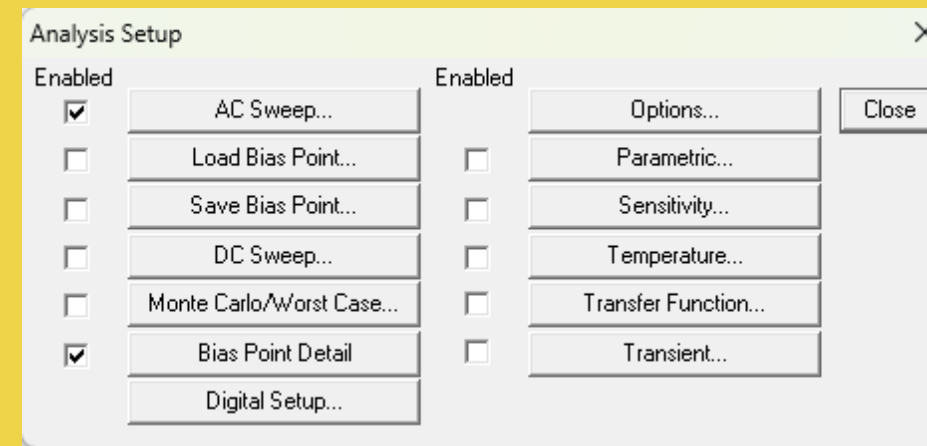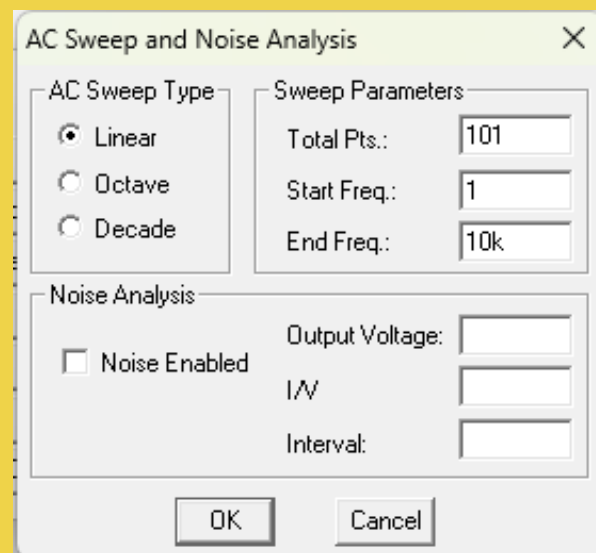

V1 (AC) = $10 \angle 0^\circ$ V;
R1 = 400 Ω ;
R2 = 10 Ω ;
C = 6.4 nF;
L = 160 mH;




3.Setting up the plot:

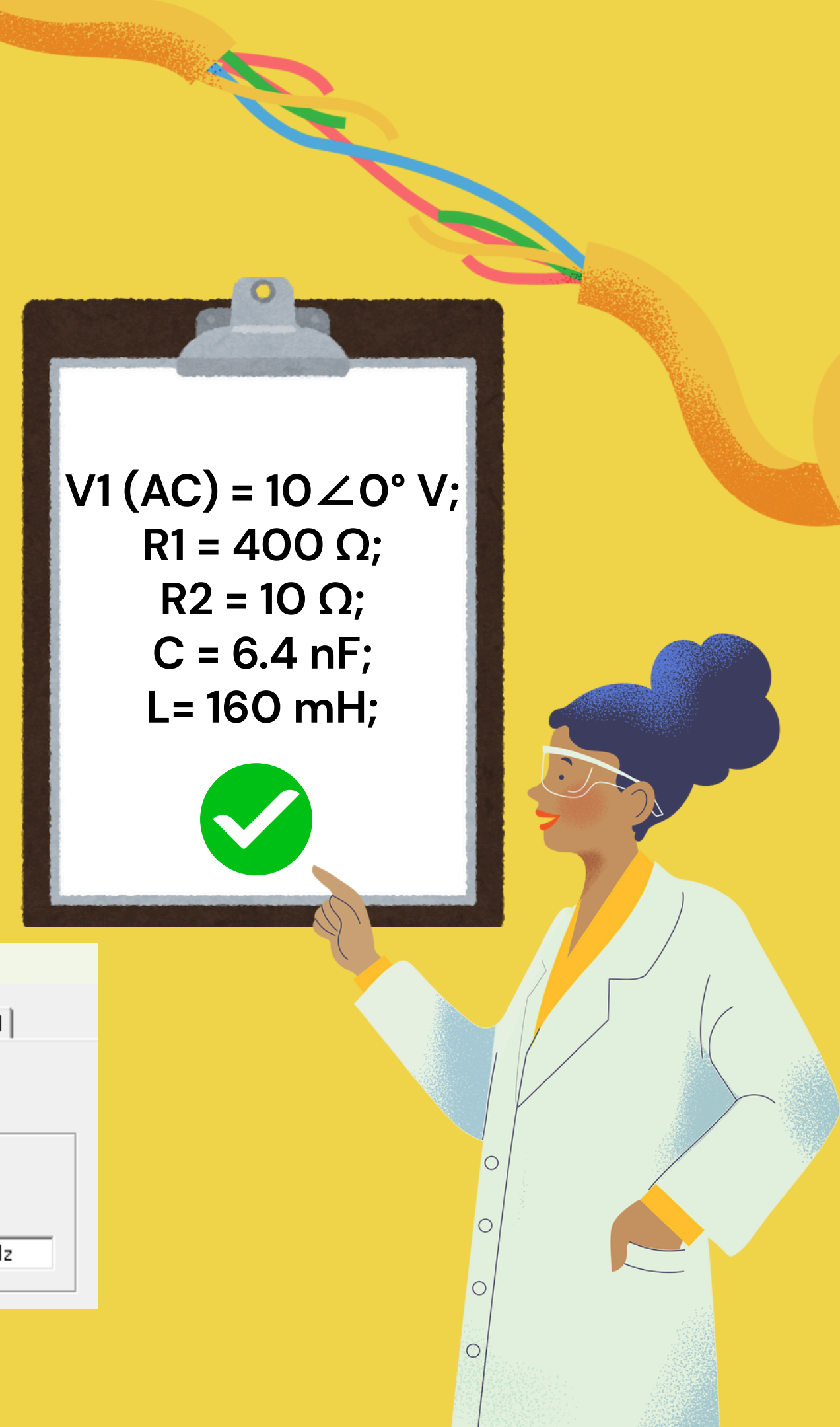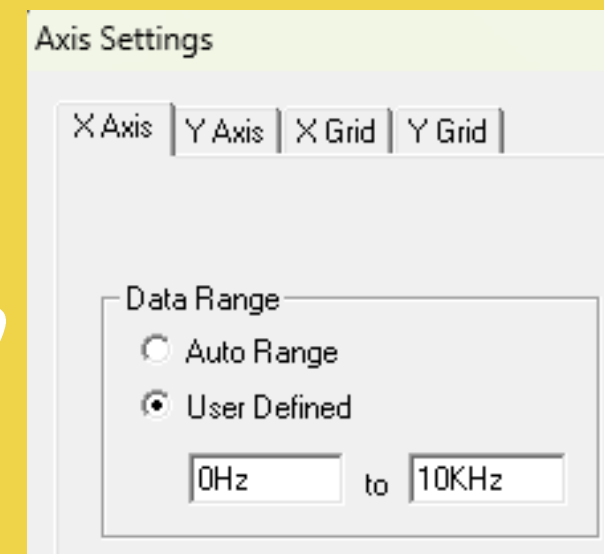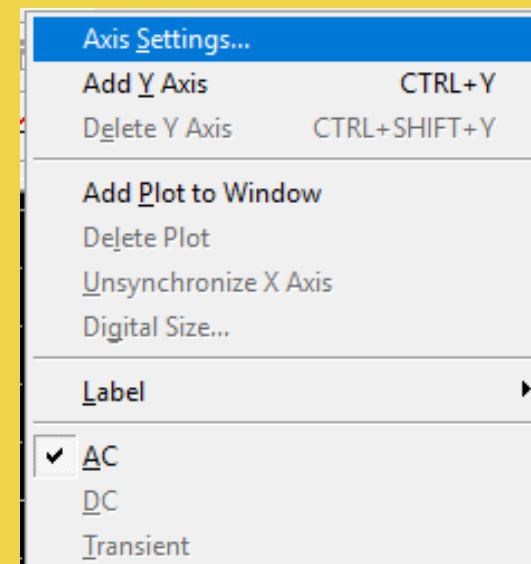

Illustrating the plot

V_o vs f

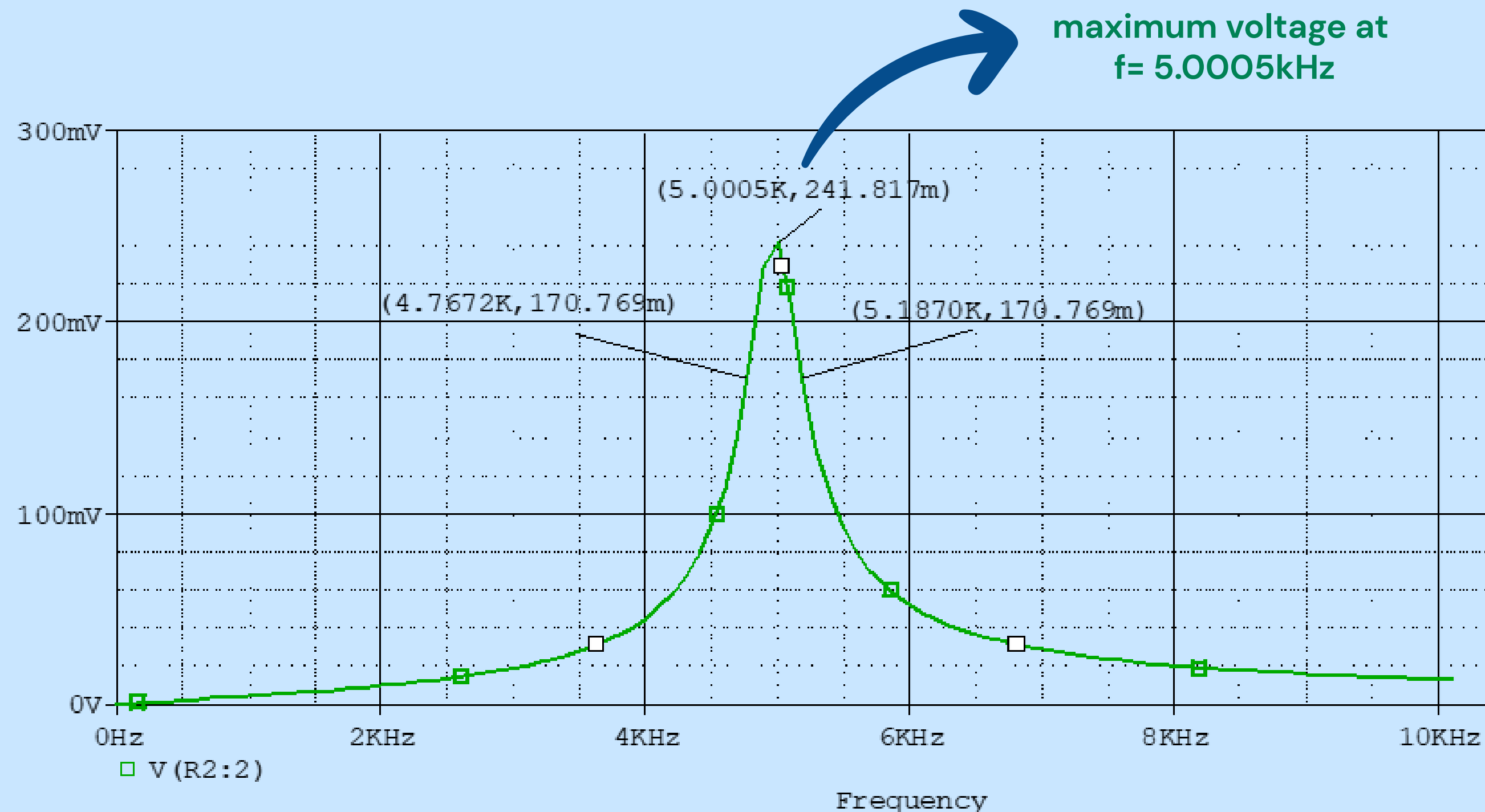A graph that plots V_o (R_2) at y axis and frequency (f) on the x axis



Here, the plot shows that, at the resonant frequency voltage on R_2 which shows that, X_L and X_C will cancel each other out, hence the resistor will remain as the only impedance in the circuit and therefore, the voltage will be at a maximum

e. Complete the following data table:

The maximum value of $ V_o $ (V)	Resonant frequency, f (kHz)	The value of the quantity that identifies the cut-off frequency	The cut-off frequency (kHz)	The Bandwidth (kHz)	Selectivity



Maximum possible output from this circuit from varying frequencies



The frequency at which the output reached its peak



Multiplying peak with 0.707 to estimate where the cut-off may be



Pinpointing the cut-off at both end using the mentioned value



Figuring a range. From low end to high end.



Quality factor Indicates how sharp the curve is

ANSWER:

V_o 0.241817 V

f 5.0005 kHz


0.707 * peak (I_o or V_o) 17.096 mA or 170.769 mV

Cut-off Freq. $f_{cl} = 4.7679$
 $f_{ch} = 5.1863$


Bandwidth 0.4184

Selectivity 11.9515

V vs f Graph

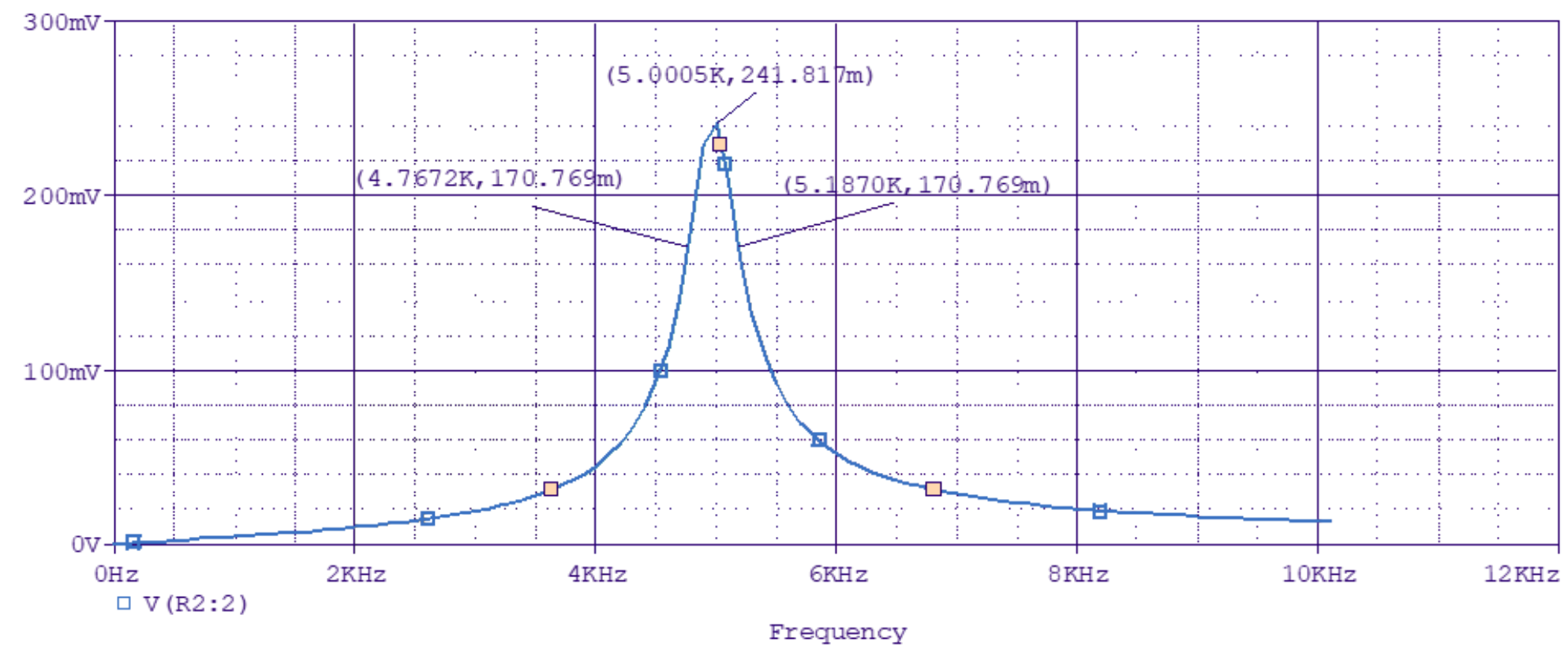

-I vs f Graph

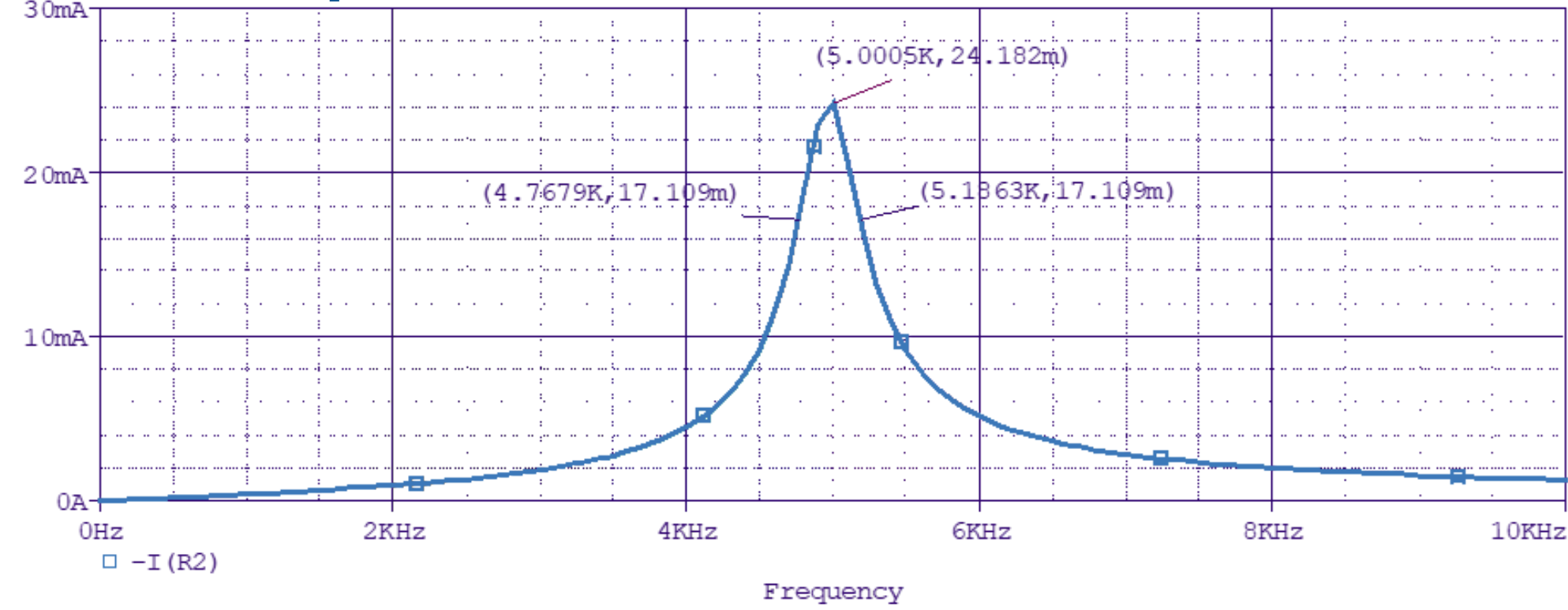

ANSWER:

V_o	0.241817 V
f	5.0005 kHz
0.707 * peak (I_o or V_o)	17.096 mA or 170.769 mV
Cut-off Freq.	$f_{cl} = 4.7679$ $f_{ch} = 5.1863$
Bandwidth	0.4184
Selectivity	11.9515

TYPES OF FILTERS

Low-pass

lets low frequencies pass, blocks high.

High-pass


lets high frequencies pass, blocks low.

Band-pass


lets only a middle range of frequencies pass.

Band-stop

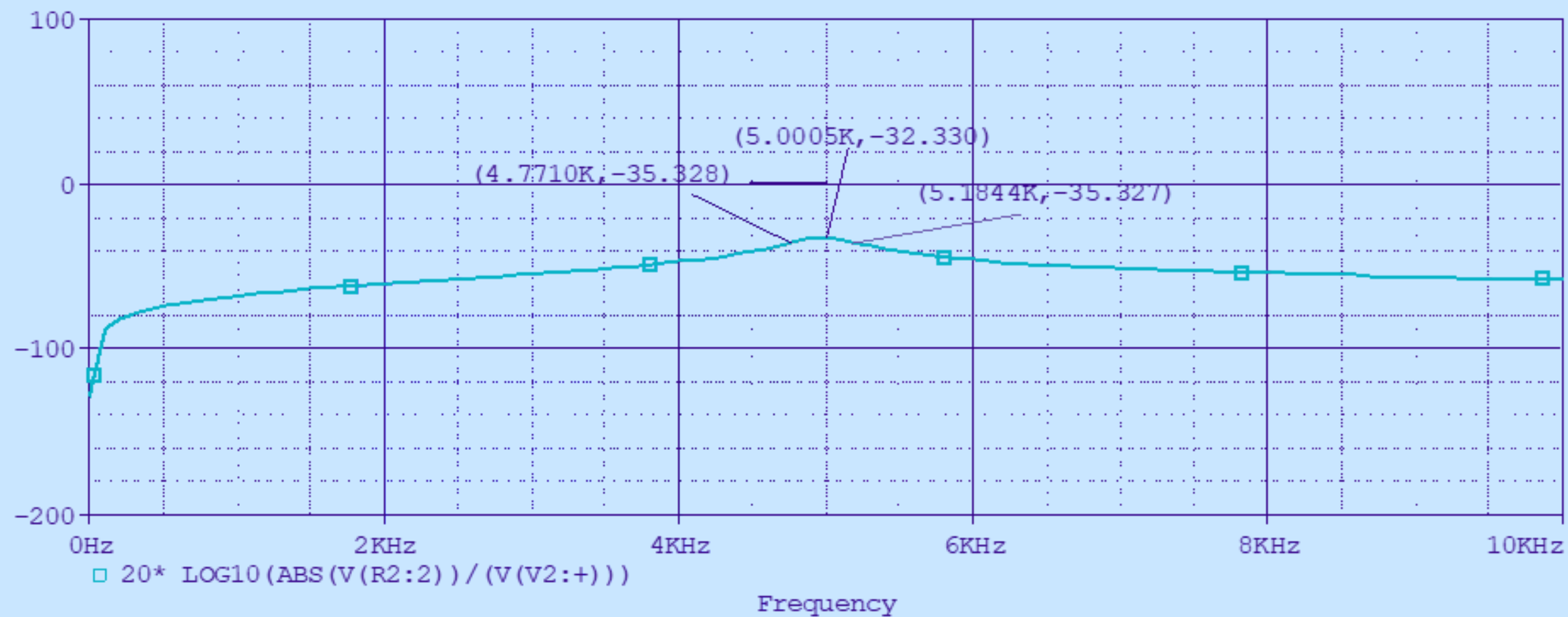blocks a middle range, lets low & high frequencies pass.



PASS-BAND & STOP-BAND

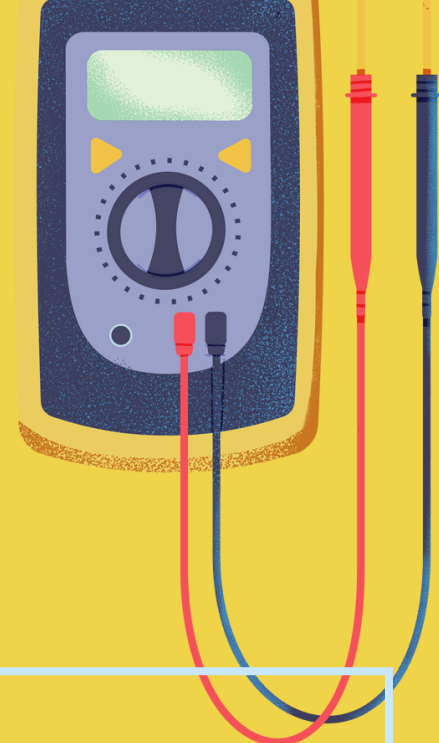

Pass-band

**Range of frequencies
where output is above
−3 dB.**

Stop-band



**Frequencies where
output is below
−3 dB.**

For our project


**Pass-band:
4.7678 kHz – 5.1863 kHz**

**Stop-band:
 $f < 4.7678$ kHz and $f > 5.1863$ kHz**

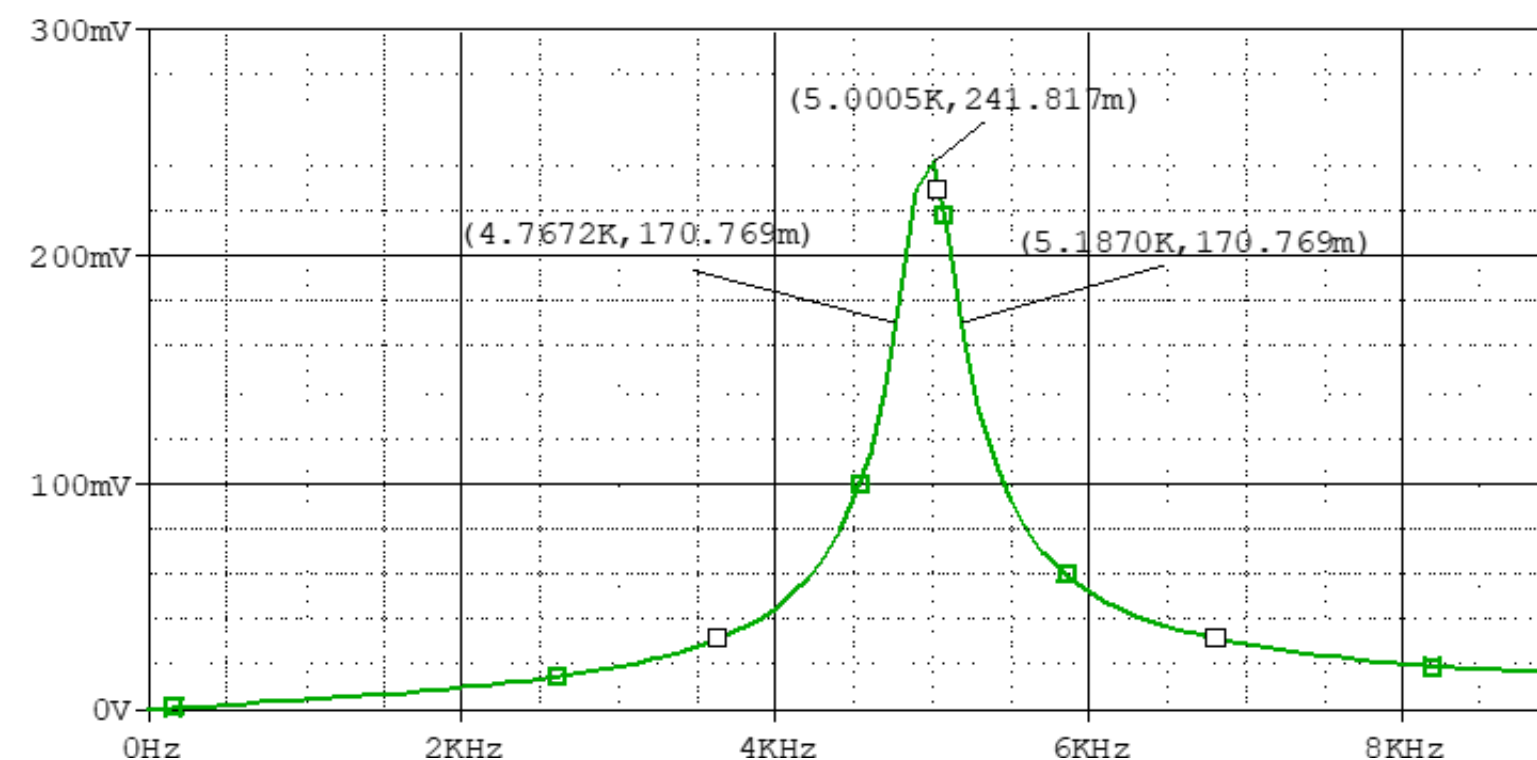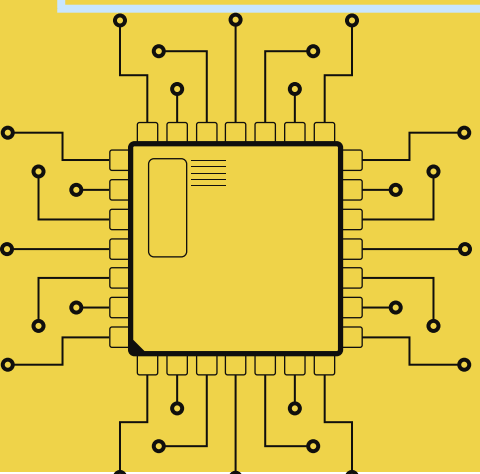
**−3 dB, 0.707 V_{max} , and 0.707 I_{max} are
equivalent because the signal is reduced to
about 70.7% of its maximum amplitude**



Graph: $|V_o|$ vs f

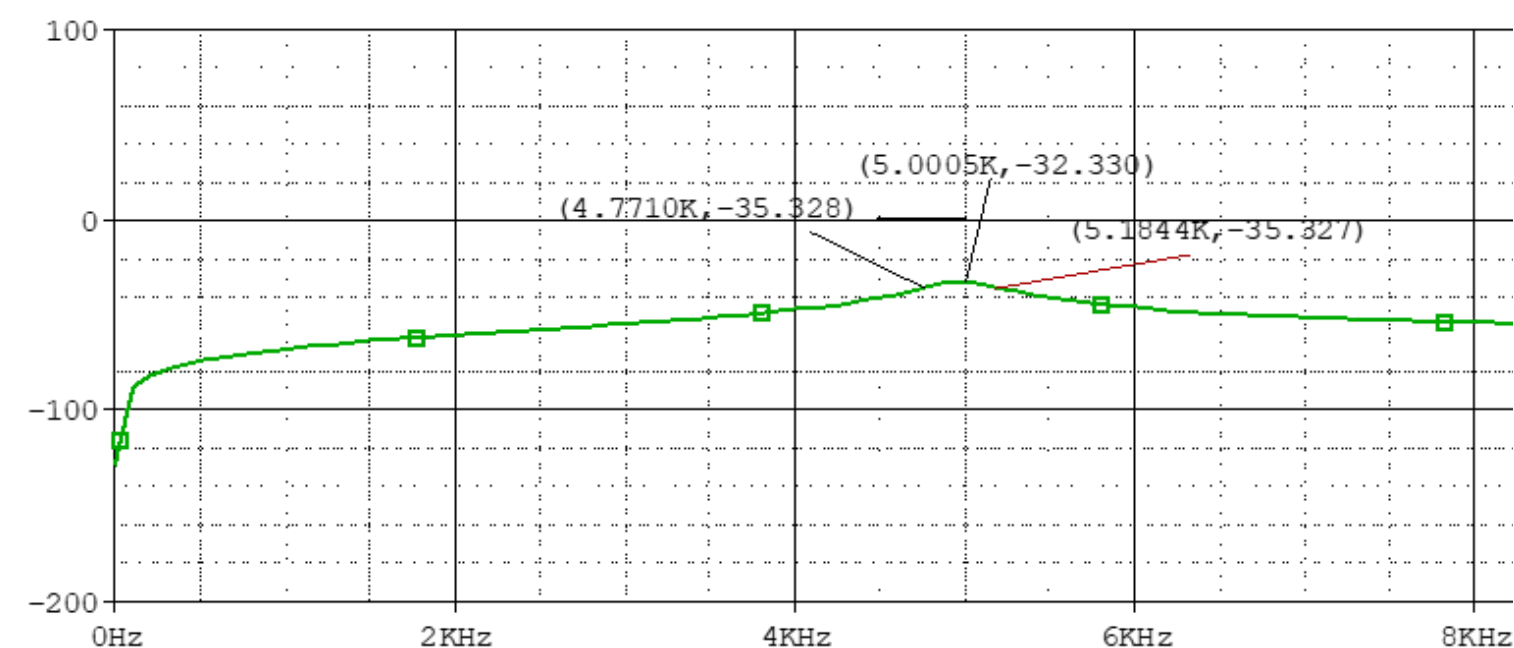




Graph: Gain(db) vs f

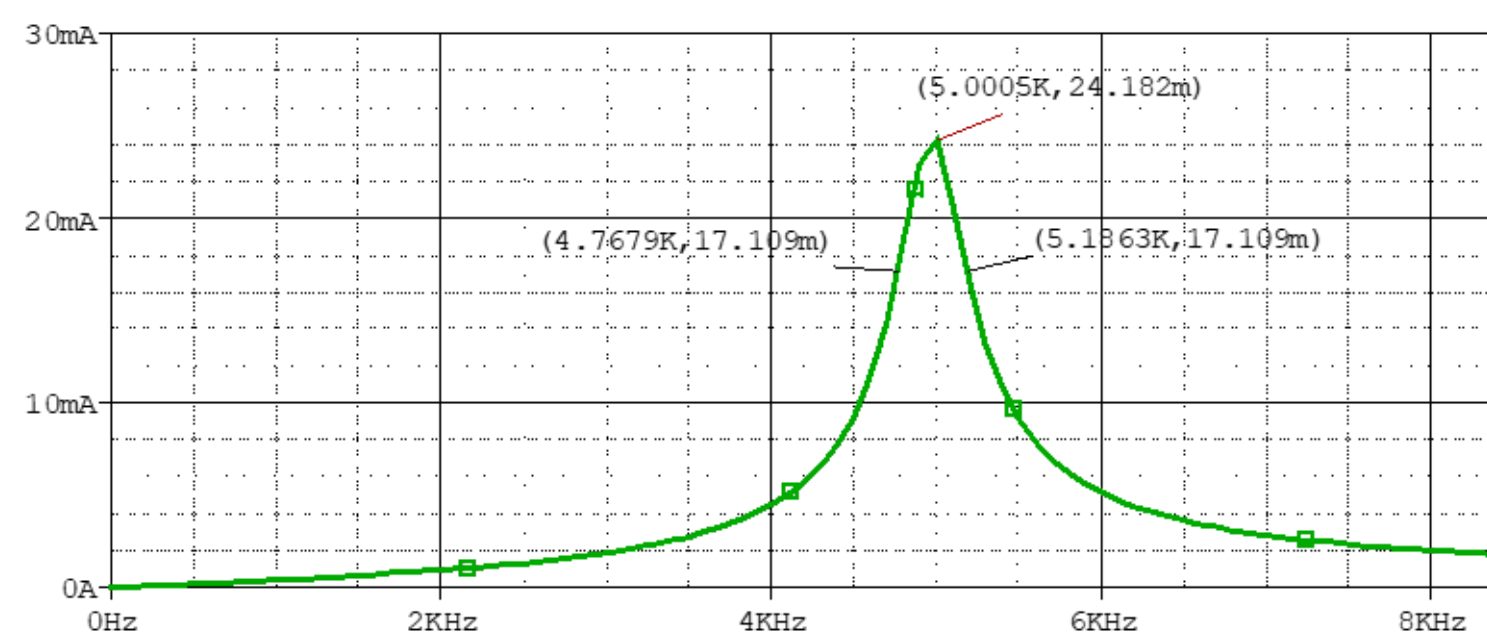


Graph: $|I_o|$ vs f

Operation of the RLC Band-pass Filter

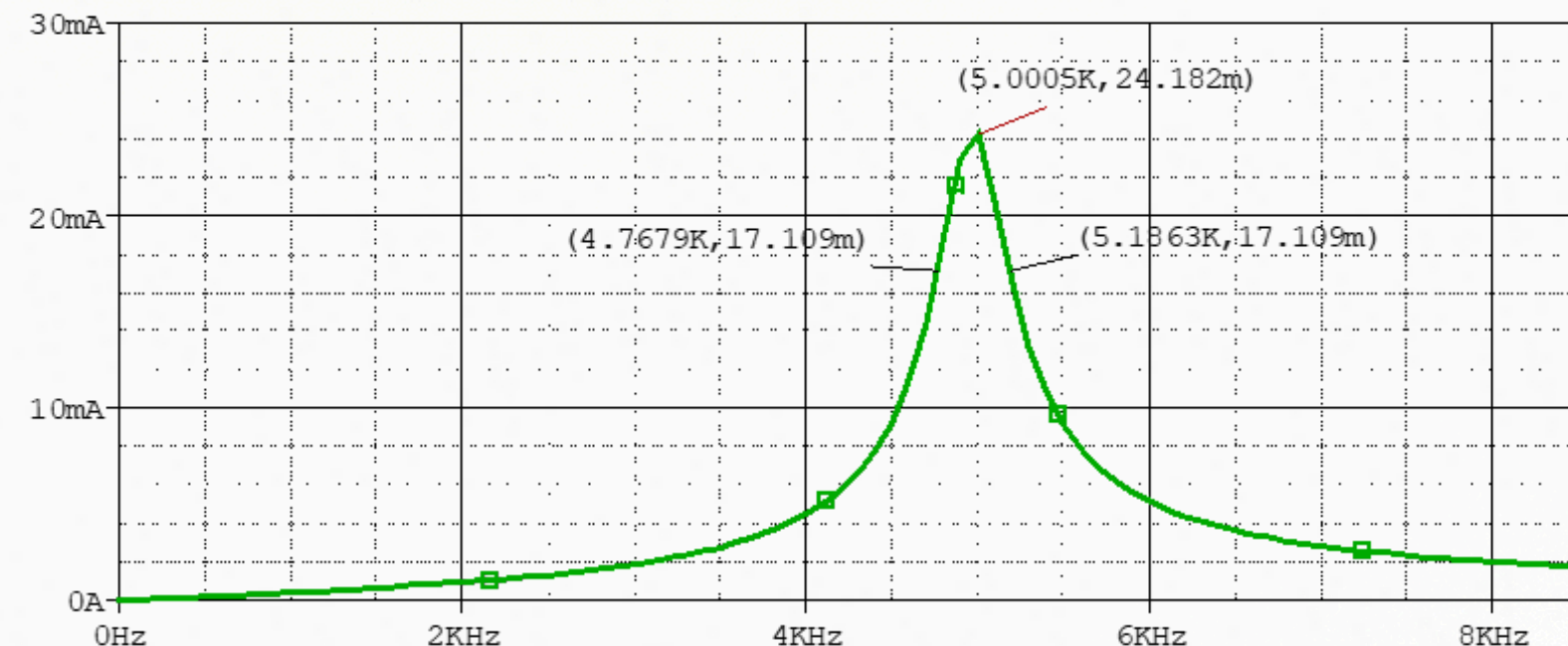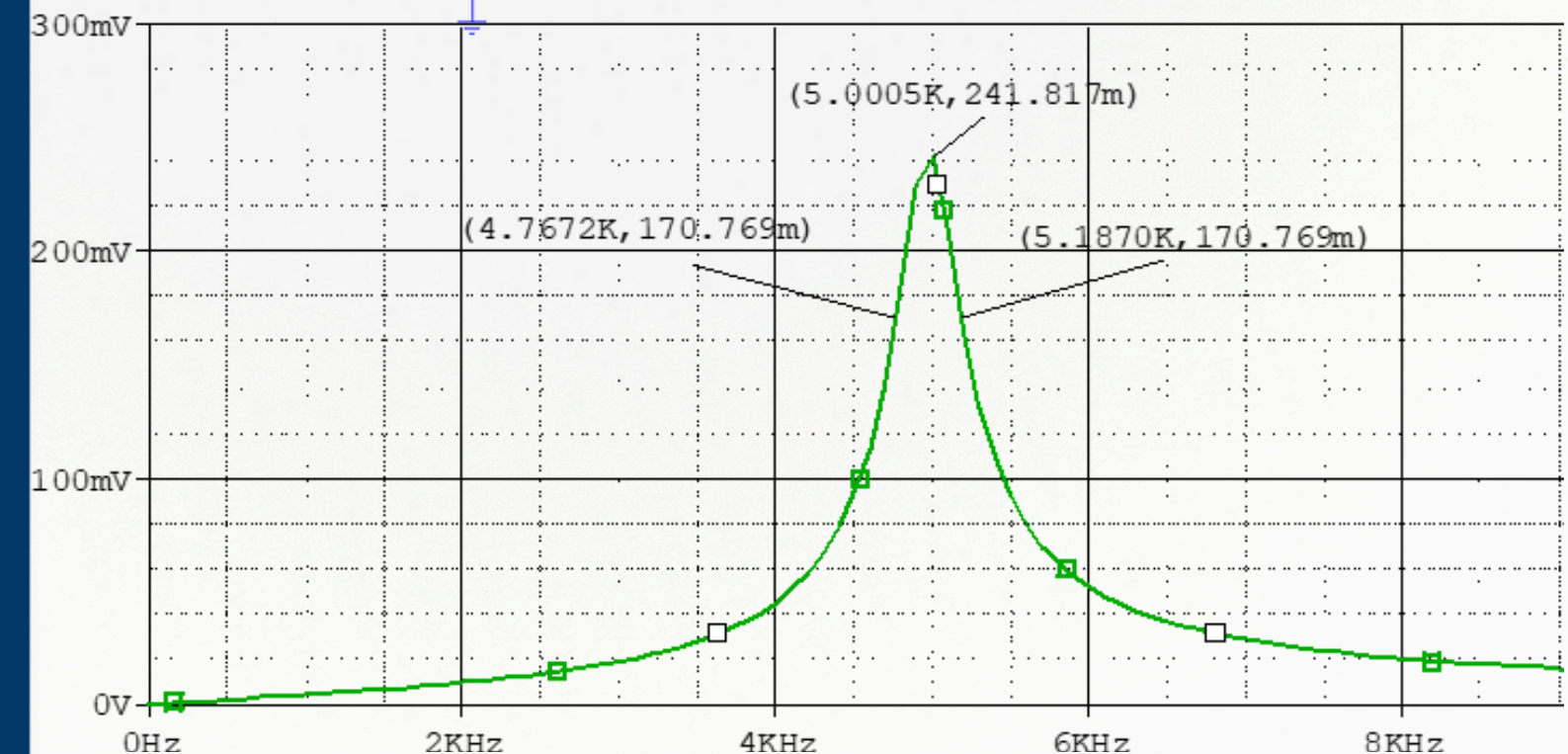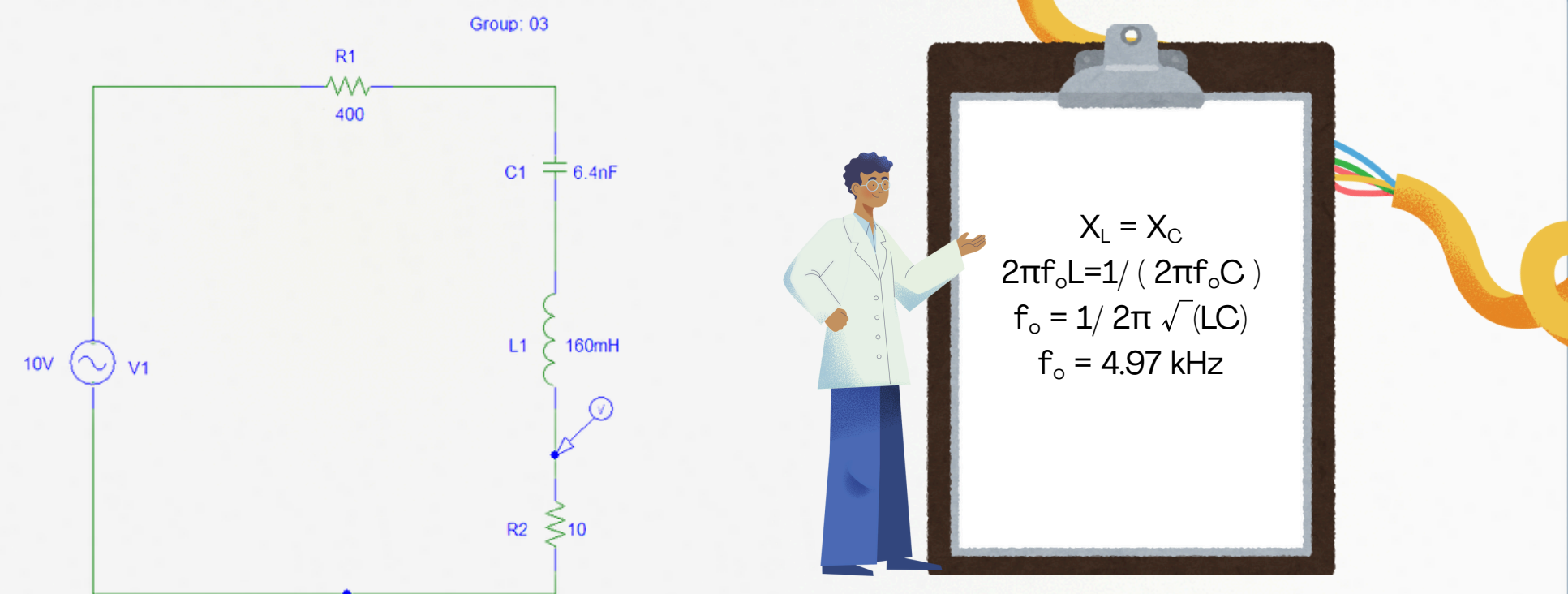- Low Frequency:
Capacitor blocks current → small output.
- High Frequency:
Inductor blocks current → small output.
- At Resonance ($f_o \approx 5.0$ kHz):
 - Reactances of L and C cancel each other.
 - Only resistive impedance remains → current is maximum.
 - Voltage across R2 is maximum.
- Bandwidth: Determined by cutoff points f_1 & f_2 (−3 dB level).



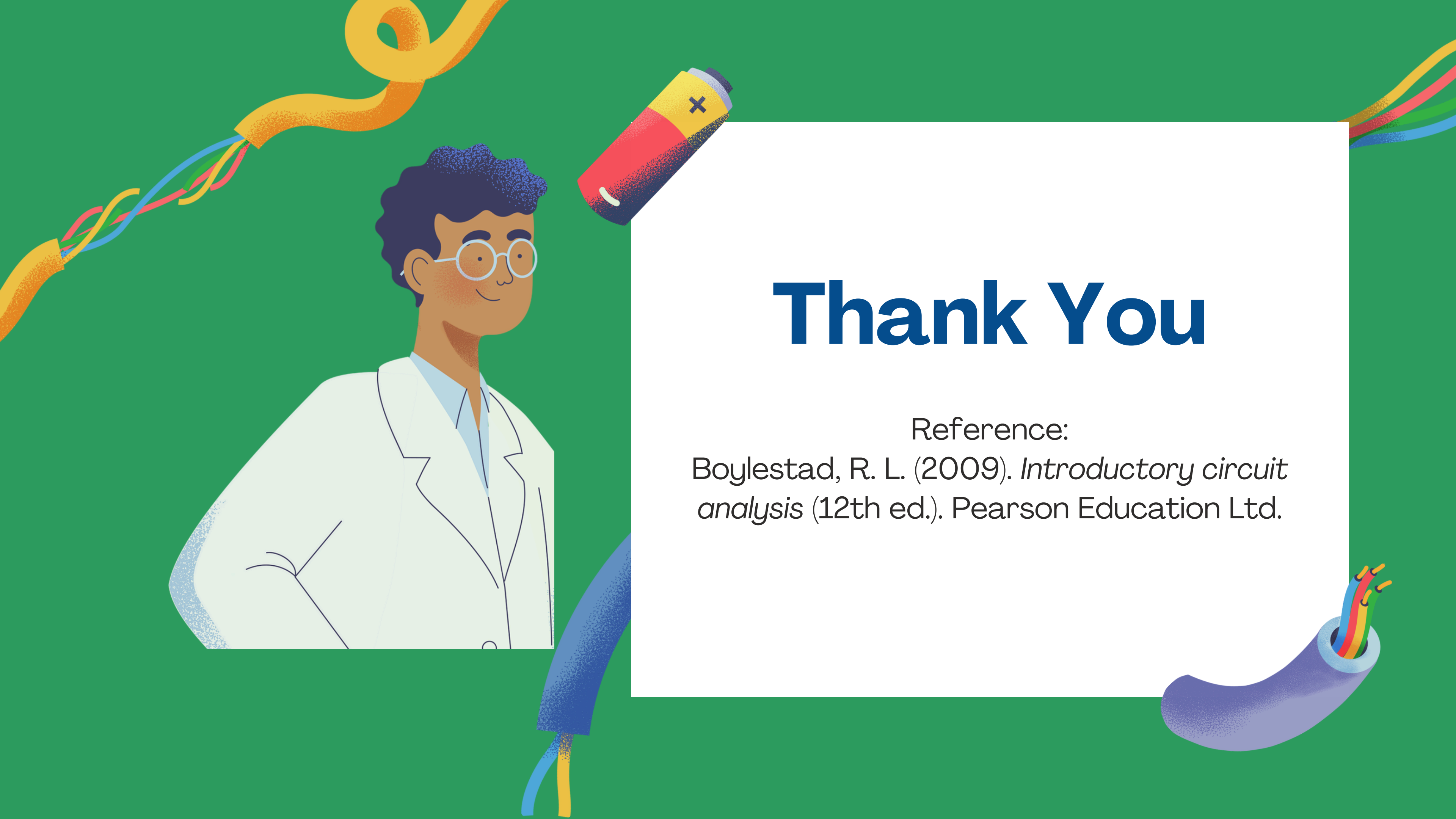An illustration on a green background featuring a scientist with dark curly hair and glasses, wearing a white lab coat, standing on the left. To the right of the scientist is a red and yellow battery with a black 'x' on its top. Several colorful wires (yellow, blue, red, green) are shown as loops and bundles around the scene. A blue cable with multiple colored wires inside is at the bottom right.

Thank You

Reference:

Boylestad, R. L. (2009). *Introductory circuit analysis* (12th ed.). Pearson Education Ltd.