

class - 5

#1] The reactance of a coil equals the resistance of a $10\text{ k}\Omega$ resistor at a frequency of 5 kHz . Determine the inductance of the coil.

2] Determine the capacitance required to establish a capacitive reactance that will match that of a 2 mH coil at a frequency of 50 kHz .

Ans

1] $X_L = \omega L$

$$X_L = 2\pi fL$$

$$L = \frac{X_L}{2\pi f} = \frac{10 \times 10^3}{2\pi \times 5 \times 10^3} = 0.32\text{ H.}$$

2]

$$X_C = X_L$$

$$\Rightarrow \frac{1}{\omega C} = \omega L$$

$$\Rightarrow C = \frac{1}{(2\pi f)^2 L} = \frac{1}{(2\pi \times 50 \times 10^3)^2 \times 2 \times 10^{-3}}$$

$$= 5\text{ nF}$$


Instantaneous and Average Power

The instantaneous power (in watts) is the power at any instant of time.

The average power (in watts) is the average of the instantaneous power over one period.

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

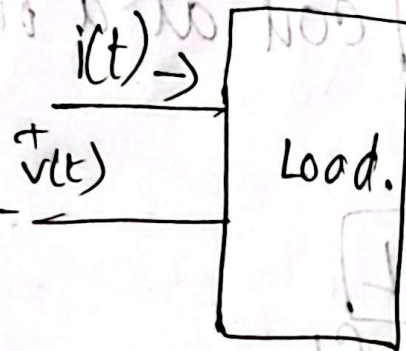

$$P(t) = v(t) i(t)$$

$$= V_m \cos(\underbrace{\omega t + \theta_v}_A) \cdot I_m \cos(\underbrace{\omega t + \theta_i}_B)$$

$$\Rightarrow \cos A \cdot \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$P(t) = \left[\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \right] + \left[\frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \right]$$

↓
instantaneous
value.
power.

Time
independent
Avg. value

Time
dependent.

$$P_{av} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$P_{av} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$= V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i)$$

$$= V_{rms} \cdot I_{rms} \cos(\theta) \quad [\theta = \theta_v - \theta_i]$$

Q) Find the instantaneous power and the avg. power absorbed by the passive linear network.

a) $v(t) = 120 \cos(377t + 45^\circ)$ volt.

$i(t) = 10 \cos(377t - 10^\circ)$ amp.

Ans

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$P_{av} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$V_m = 120$$

$$I_m = 10$$

$$\theta_v = 45^\circ$$

$$\theta_i = -10^\circ$$

$$P_{av} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{120 \times 10}{2} \cos(45^\circ - (-10^\circ))$$

$$= \underline{\underline{344.15 \text{ W}}}$$

Q Instantaneous power

$$p(t) = v(t) i(t)$$

$$= 120 \cos(377t + 45^\circ) \cdot 10 \cos(377t - 10^\circ)$$



$$\# \cos A \cdot \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$= 120 \times 10 \times \frac{1}{2} \times \cos(55^\circ) + 120 \times 10 \times \frac{1}{2} \times$$

$$\cos(2 \times 377t + 45^\circ - 10^\circ)$$

$$= \underline{\underline{344.15 + 600 \cos(754t + 35^\circ) \text{ watt}}}$$

Ans

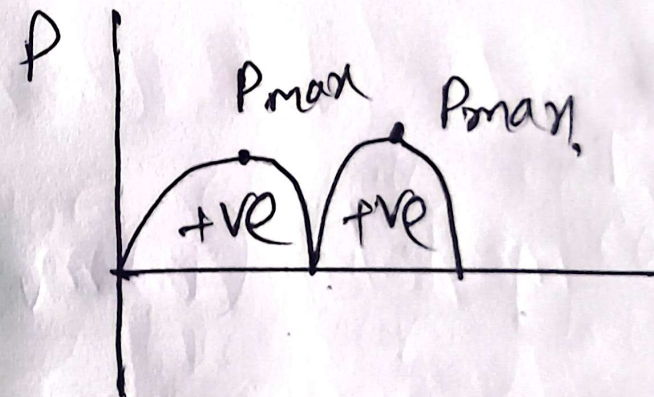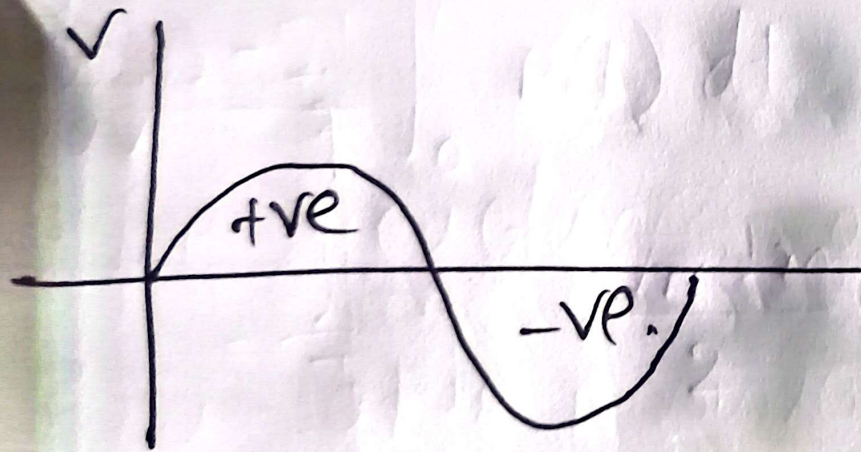

for
power.