

Lab Report  
Summer 2025

Course Code: **EEE203L**  
Course Title: **Electronic Circuits II Laboratory**

Lab Section: **02**

**Experiment No.: 2**

**Name of the experiment: verification of KVL in AC circuit**

**Date of Submission:**

***Group No: 3***

**Group Member Details:**

1.    *Name:*        **Souvik Barman Ratul**  
      *I.D.*            **24121205**
2.    *Name:*        **Oshiul Alim Ornob**  
      *I.D.*            **24121268**
3.    *Name:*        **Mahdi Zaman**  
      *I.D.*            **24121307**
4.    *Name:*        **Alif Tamjid**  
      *I.D.*            **24121308**

**Submitted By :**

Name : Souvik Barman Ratul

**Submitted To :**

Saad Mahbub Chowdhury

I.D. : 24121205

Compilation of result and Calculations (with ckt diagram and verification of result):

**Circuit Diagram:**

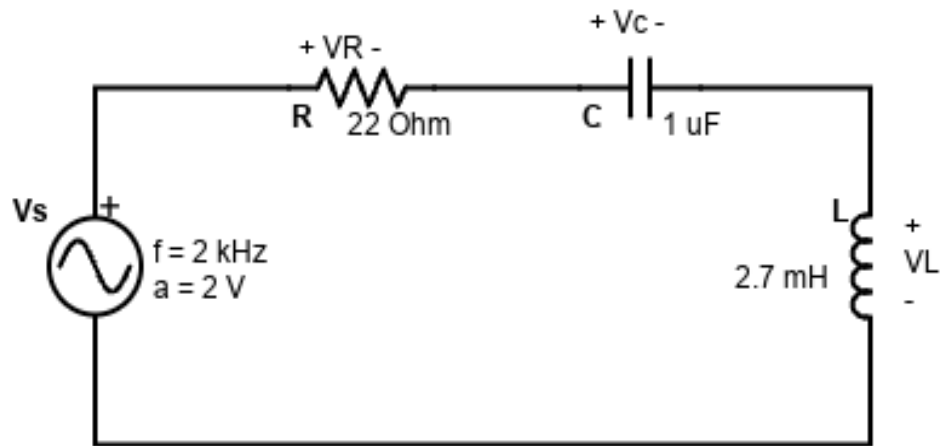


Figure 1

## Data Sheet :

**Table For  $V_s$**

| $V_{Sa}$ (V)<br>(Peak value from<br>Oscilloscope) | $ V_s  = V_{Sa} / \sqrt{2}$<br>(V) | F (kHz)<br>(From Oscilloscope) | $\angle V_s$<br>(0) |
|---------------------------------------------------|------------------------------------|--------------------------------|---------------------|
| 2                                                 | 1.414                              | 1.99                           | 0                   |

**Table For  $V_R$**

| $V_{Ra}$ (V)<br>(Peak value<br>from<br>Oscilloscope) | $ V_R  =$<br>$V_{Ra} / \sqrt{2}$<br>(V) | Sign (+/-) | $\Delta t$ (ms)<br>(From<br>Oscilloscope) | F (kHz)<br>(From<br>Oscilloscope) | $360f\Delta t$<br>(0) | $\angle V_R$<br>(0) |
|------------------------------------------------------|-----------------------------------------|------------|-------------------------------------------|-----------------------------------|-----------------------|---------------------|
| 0.74                                                 | 0.523                                   | (+)        | 0.078                                     | 1.99                              | 55.879                | +55.879             |

**Table For  $V_C$**

| $V_{Ca}$ (V)<br>(Peak value<br>from<br>Oscilloscope) | $ V_C  =$<br>$V_{Ca} / \sqrt{2}$<br>(V) | Sign (+/-) | $\Delta t$ (ms)<br>(From<br>Oscilloscope) | F (kHz)<br>(From<br>Oscilloscope) | $360f\Delta t$<br>(0) | $\angle V_C$<br>(0) |
|------------------------------------------------------|-----------------------------------------|------------|-------------------------------------------|-----------------------------------|-----------------------|---------------------|
| 2.62                                                 | 1.853                                   | (-)        | 0.206                                     | 1.99                              | 147.578               | -147.578            |

**Table For  $V_L$**

| $V_{La}$ (V)<br>(Peak value<br>from<br>Oscilloscope) | $ V_L  =$<br>$V_{La} / \sqrt{2}$<br>(V) | Sign (+/-) | $\Delta t$ (ms)<br>(From<br>Oscilloscope) | F (kHz)<br>(From<br>Oscilloscope) | $360f\Delta t$<br>(0) | $\angle V_L$<br>(0) |
|------------------------------------------------------|-----------------------------------------|------------|-------------------------------------------|-----------------------------------|-----------------------|---------------------|
| 1.07                                                 | 0.7566                                  | (+)        | 0.180                                     | 1.99                              | 128.95                | +128.95             |

**Table For  $V_R + V_C + V_L$**

| $ V_R + V_C + V_L $<br>(V)      | $\angle V_R + V_C + V_L$<br>(°)     |
|---------------------------------|-------------------------------------|
| (0.523+1.853+0.756j)<br>=3.1326 | (+55.879-147.578+128.95)<br>=37.251 |

$$\text{Error} = \{ (|V_R + V_C + V_L| - |V_S|) / (|V_R + V_C + V_L|) \} \times 100\%$$

$$= \{ (3.1326 - 1.414) / 3.1326 \} \times 100\%$$



$$= 54.86\%$$

# Classwork Proof :


$V_s$




$V_R$

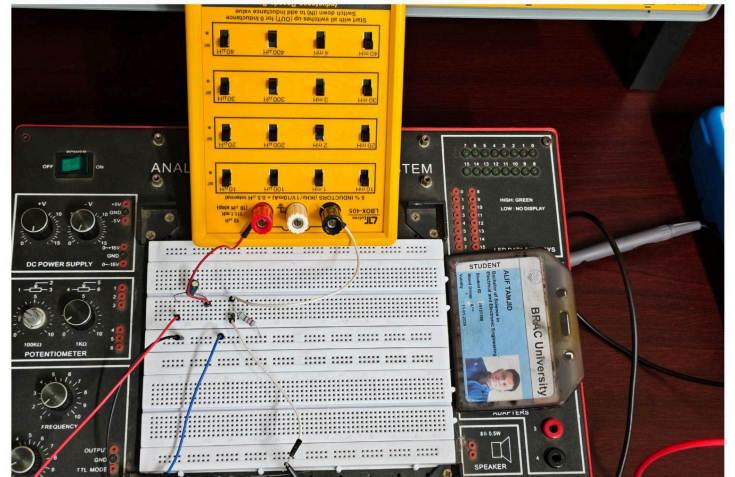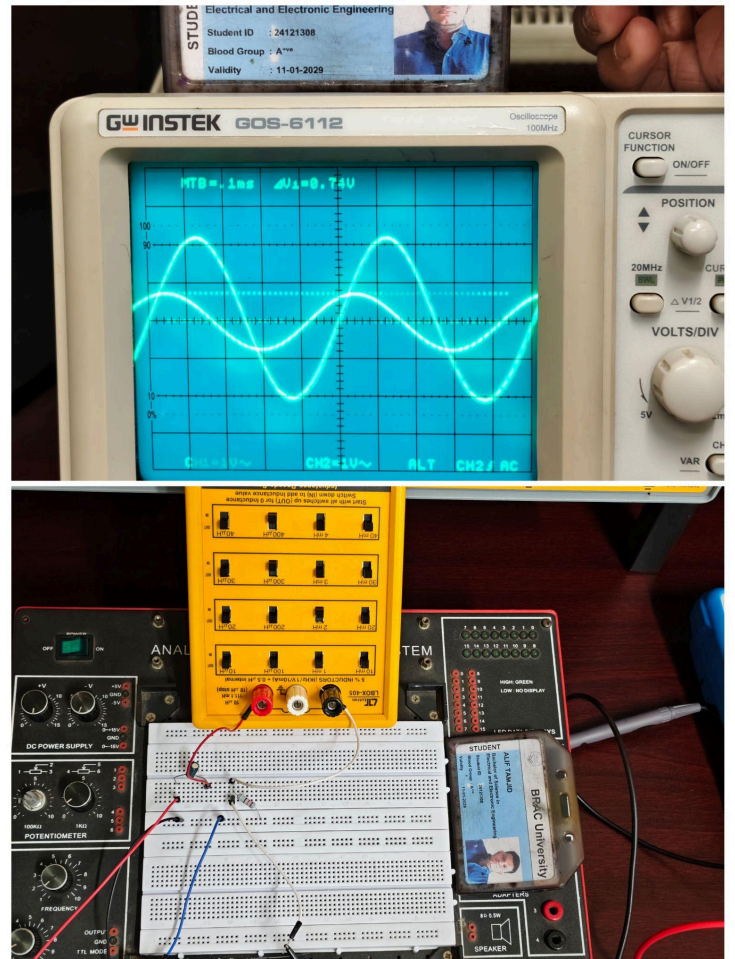

$V_c$

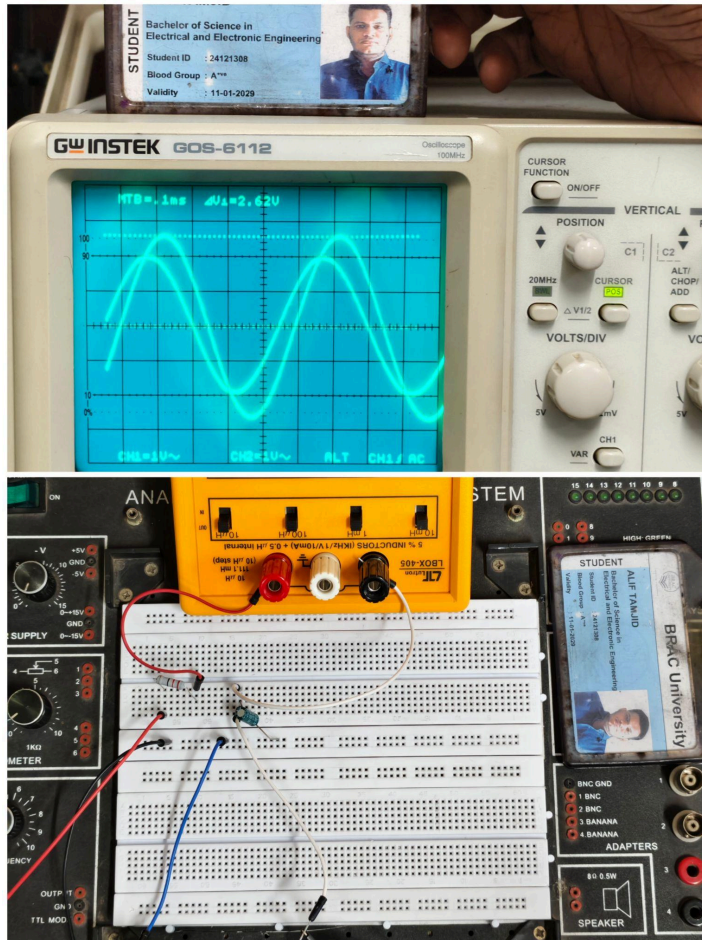

$V_L$

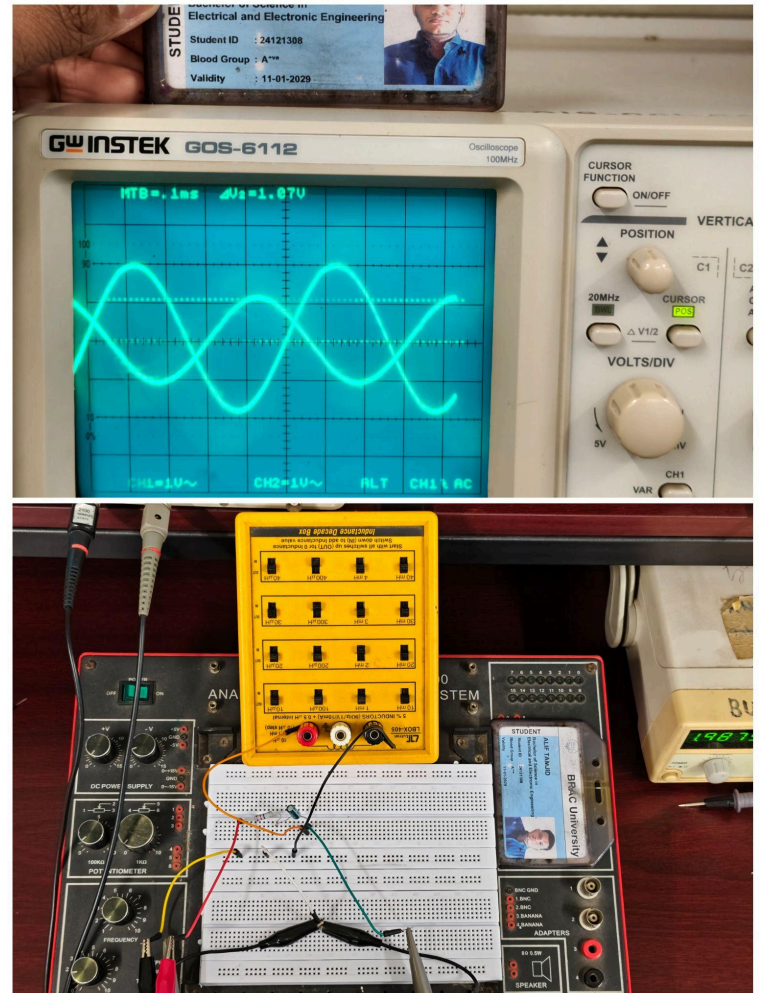



## Appendix:

**Brac University**  
**Department of Electrical & Electronic Engineering (EEE)**  
**EEE203L – Electrical Circuits II Laboratory**

**Experiment 2**


**Name of the Experiment:**

**Verification of KVL in AC Circuits**

**Objective:**

The objective of this experiment is to study RLC series circuit when energized by an ac source. KVL in phasor form will also be verified.

**Circuit Diagram:**

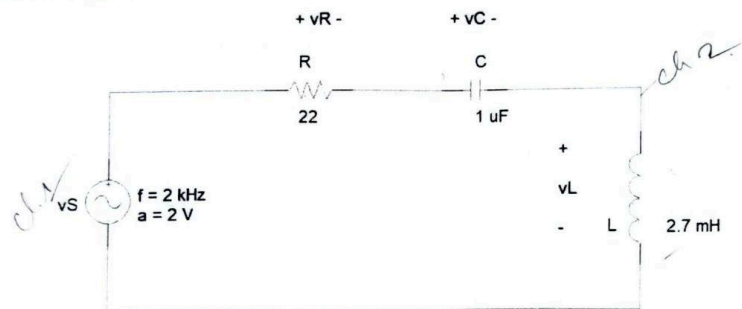

**Figure 1 : KVL circuit**

**Equipments:**

1. Multimeter
2. AC ammeter
3. Resistances –  $22\Omega$  (1 piece) and  $2.5k\Omega$  (3 pieces)
4. Capacitor –  $1\mu F$  (1 piece)
5. Inductor –  $2.7\text{ mH}$  (1 piece)
6. Bread Board
7. Wires for connection

**Procedure:**

1. Construct the circuit as shown in figure 1.
2. Observe the wave shapes for the voltages of  $V_R$ ,  $V_L$ , and  $V_C$  and fill up the required table.

**Data:**

| Table for $V_s$                                |                                          |                                |                     |
|------------------------------------------------|------------------------------------------|--------------------------------|---------------------|
| $V_{sa}$ (V)<br>(Peak value from Oscilloscope) | $ V_s  = \frac{V_{sa}}{\sqrt{2}}$<br>(V) | f (kHz)<br>(From oscilloscope) | $\angle V_s$<br>(o) |
| 2. V                                           | 1.414                                    | 1.99                           | 0                   |

| Table for $V_R$                                |                                          |            |                                        |                               |                       |                     |
|------------------------------------------------|------------------------------------------|------------|----------------------------------------|-------------------------------|-----------------------|---------------------|
| $V_{Ra}$ (V)<br>(Peak value from Oscilloscope) | $ V_R  = \frac{V_{Ra}}{\sqrt{2}}$<br>(V) | Sign (+/-) | $\Delta t$ (ms)<br>(From oscilloscope) | f(kHz)<br>(From oscilloscope) | $360f\Delta t$<br>(o) | $\angle V_R$<br>(o) |
| 0.74                                           | 0.523                                    | (+)        | 0.078                                  | 1.99                          | 55.879                | +52.879             |

| Table for $V_C$                                |                                          |            |                                        |                               |                       |                     |
|------------------------------------------------|------------------------------------------|------------|----------------------------------------|-------------------------------|-----------------------|---------------------|
| $V_{Ca}$ (V)<br>(Peak value from Oscilloscope) | $ V_C  = \frac{V_{Ca}}{\sqrt{2}}$<br>(V) | Sign (+/-) | $\Delta t$ (ms)<br>(From oscilloscope) | f(kHz)<br>(From oscilloscope) | $360f\Delta t$<br>(o) | $\angle V_C$<br>(o) |
| 2.62                                           | 1.853                                    | (-)        | 0.206                                  | 1.99                          | 147.578               | -147.578            |

| Table for $V_L$                                |                                          |            |                                        |                               |                       |                     |
|------------------------------------------------|------------------------------------------|------------|----------------------------------------|-------------------------------|-----------------------|---------------------|
| $V_{La}$ (V)<br>(Peak value from Oscilloscope) | $ V_L  = \frac{V_{La}}{\sqrt{2}}$<br>(V) | Sign (+/-) | $\Delta t$ (ms)<br>(From oscilloscope) | f(kHz)<br>(From oscilloscope) | $360f\Delta t$<br>(o) | $\angle V_L$<br>(o) |
| 1.07                                           | 0.7566                                   | (+)        | 0.180                                  | 1.99                          | 128.95                | +128.95             |

| Table for $V_R + V_C + V_L$ |                                 |
|-----------------------------|---------------------------------|
| $ V_R + V_C + V_L $<br>(V)  | $\angle V_R + V_C + V_L$<br>(o) |
| 3.1326                      | 37.251                          |

*Handwritten signature*  
13/02/25



## **Conclusion:**

We built a circuit using a resistor, capacitor, and inductor all in a line. Then we sent wave-like electricity (AC) through it and measured how the waves changed in each part. We added up the voltages (and their wave angles) from all the parts and compared it to the total voltage from the source. We found that:

1. The total we got was close to what we expected.
2. There was some error (about 54.86%), maybe because of mistakes while measuring or because real parts do not behave perfectly.

So, even though we had some small differences, the experiment mostly matched what KVL said should happen. That means KVL works in AC circuits, just like in normal ones, but we need to be careful with phase angles.